



COE211: Digital Logic Design

Memory Devices



Outline

- Random Access Memory (RAM)
 - Read and write operations
 - RAM construction
 - RAM addressing
 - Types of RAM

- Read Only Memory (ROM)
 - Types of ROM
 - Implementing Functions using PROM



Memories

- A memory unit is a device to which binary information is transferred for storage and from which information is retrieved when needed for processing.
- Different memory types:
 - Technology: magnetic, voltage, charge, fuse
 - Volatility: volatile, non-volatile
 - Access sequence: random, sequential
 - Speed: access time and throughput
- Memory access types:
 - Random Access Memory (RAM)
 - Read Only memory (ROM)
- Is memory combinational or sequential logic?
 - RAM: similar to register, based on FFs, but have no clock
 - ROM: combinational (programmable logic)



Memory Layout

- Example:

- 1024 16-bit word storage
- 10 bits identify address
- 16 bits stored at each location


- Why not make memory bit-wise addressable?

- How many bits would it have?
- How many address lines?
- How big a decoder?

- Remember:

- k (Kilo) = 2^{10}
- M (Mega) = 2^{20}
- G (Giga) = 2^{30}


Memory address	
Binary	Decimal
0000000000	0
0000000001	1
0000000010	2
	⋮
1111111101	1021
1111111110	1022
1111111111	1023

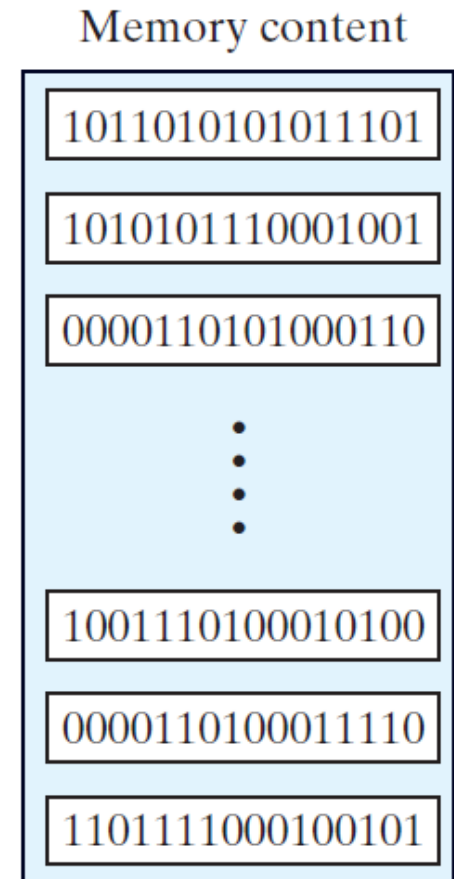



Random-access Memory (RAM)

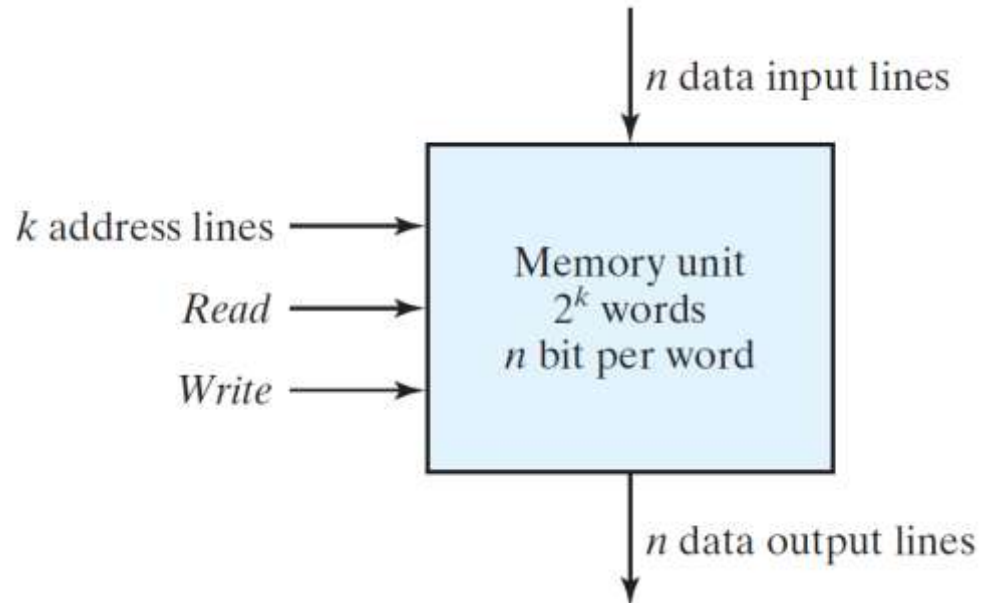
- Memory terminology:
 - Smallest unit is "word" (n bits wide)
 - Identified by "address"
- Block diagram:
 - k address lines
 - At most 2^k words storage
 - n data lines (input and output)
- What is the total memory size in bits?
 - Size = $2^k \times n$ bits
- Example:
 - 1024-bit memory with 16-bit words
 - How many address lines?





RAM Read and Write Operations

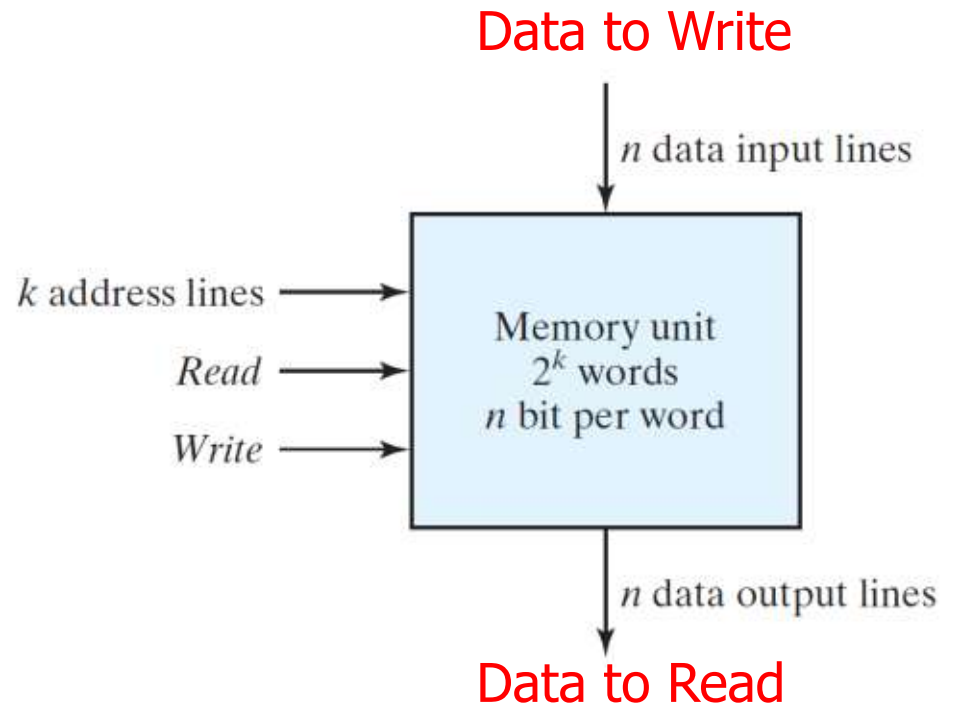- Control inputs:
 - Address
 - Read
 - Write
- Write operation
 1. Apply address to address lines
 2. Apply data to data input lines
 3. Activate write input
- Read operation
 1. Apply address to address line
 2. Activate read input
 3. Read value from data output lines





Read and Write Operations (Cont'd)

- Control inputs on commercial memories
 - Memory enable
 - Read and write
- What timing constraints need to be considered?
 - *Access time*: time to select a word and read it
 - *Cycle time*: time to complete a write operation
 - Also: setup and hold time on address lines


Control Inputs to Memory Chip

Memory Enable	Read/Write	Memory Operation
0	X	None
1	0	Write to selected word
1	1	Read from selected word




Memory Cell Design

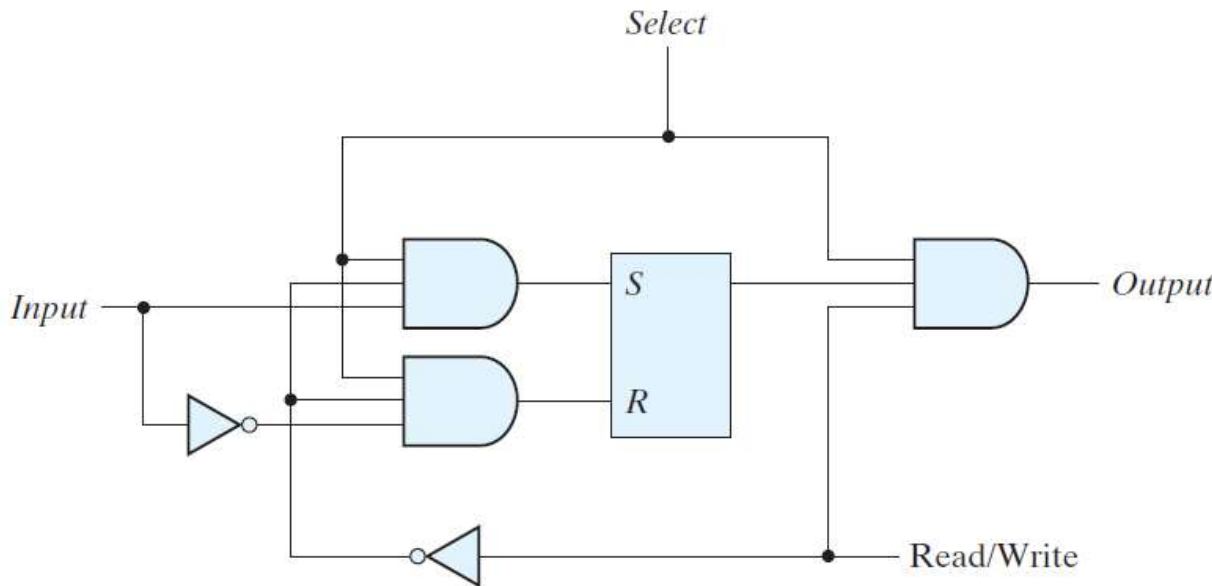- Binary memory cell implemented with SR latch:
(Note: memory is not clocked)



(a) Logic diagram

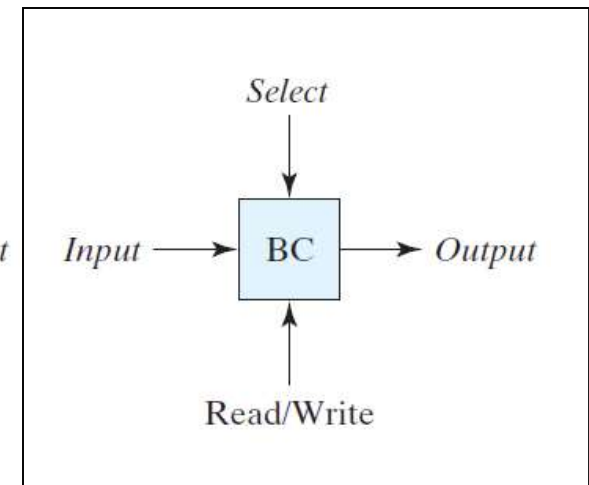


(b) Block diagram





Internal RAM Construction

- Internal layout of memory:
 - One word per "row"
 - Each "binary cell" stores one bit

- Memory cell:

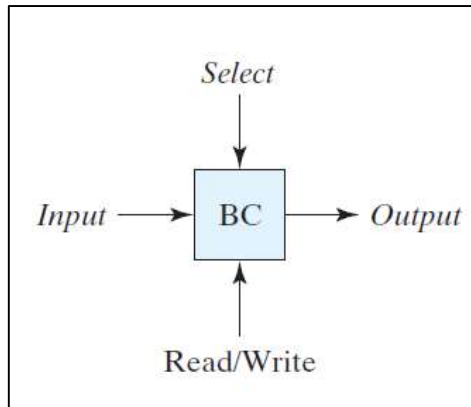

- Decoder:
 - Selects word

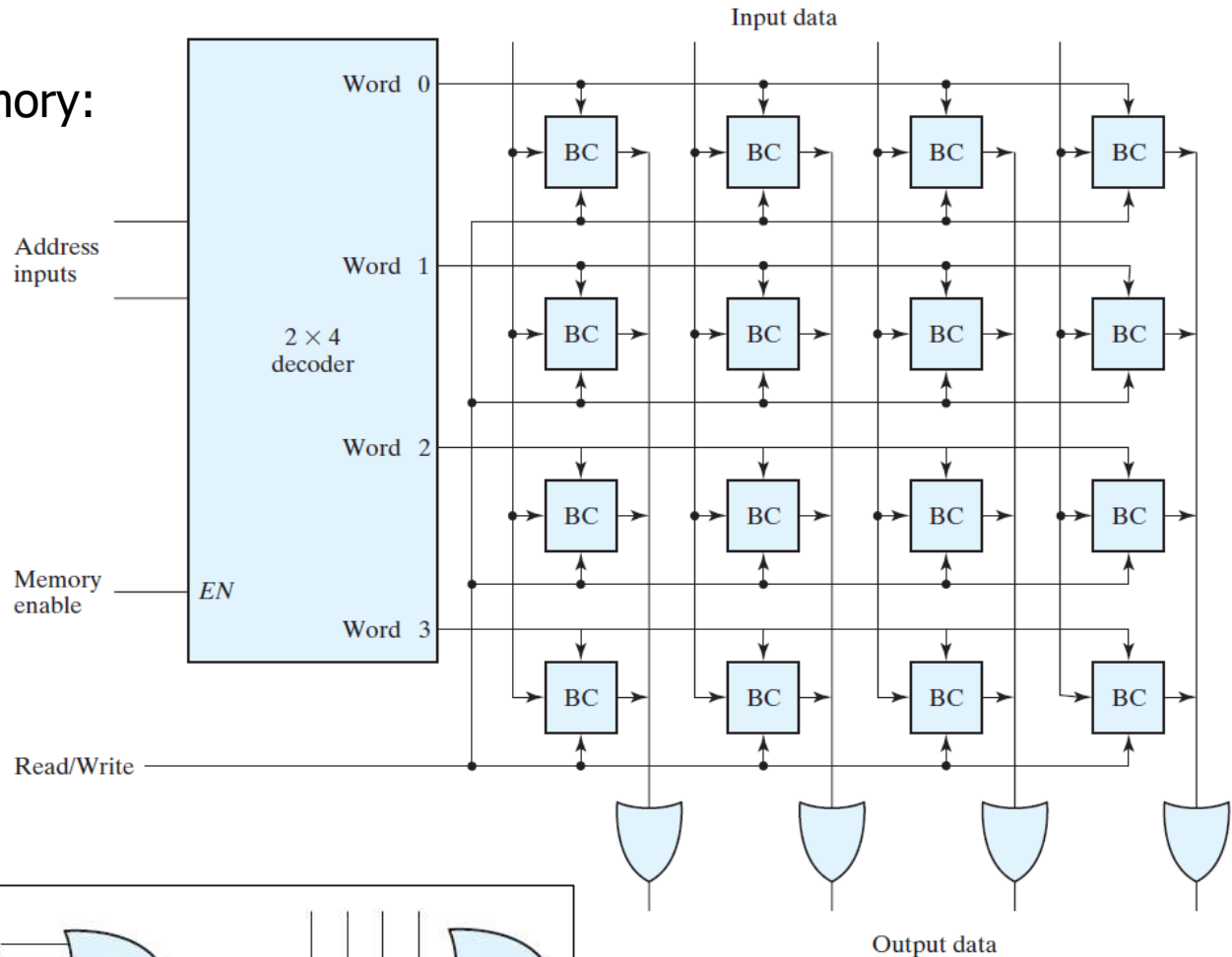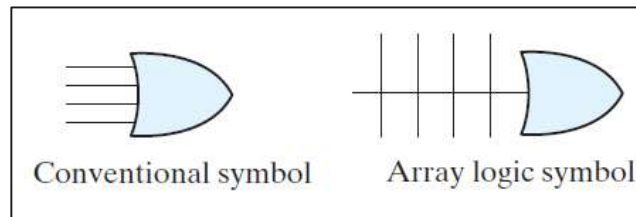



Types of RAM


- **Static Random Access Memory (SRAM)**
 - Operates like a collection of latches
 - Once a value is written, it is guaranteed to remain in the memory as long as power is applied
 - Generally expensive
 - Used inside processors

- **Dynamic Random Access Memory (DRAM)**
 - Generally, simpler internal design than SRAM
 - Requires data to be rewritten (refreshed), otherwise data is lost
 - Often hold larger amount of data than SRAM
 - Longer access times than SRAM
 - Used as main memory in computer systems




Read-Only Memory (ROM)

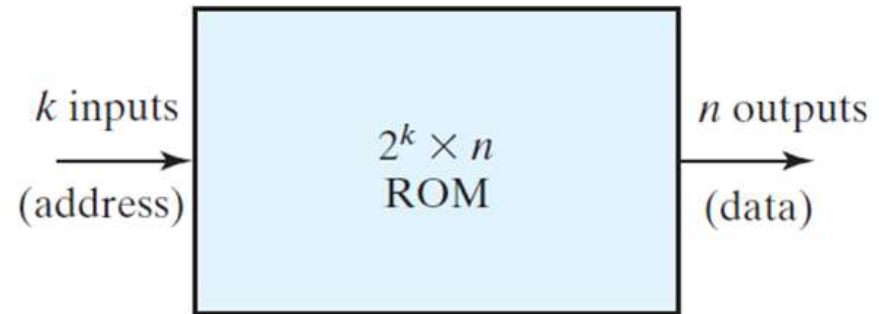- Storage for memory that does not need to change
- Block diagram:
 - Address
 - Outputs
 - No data inputs



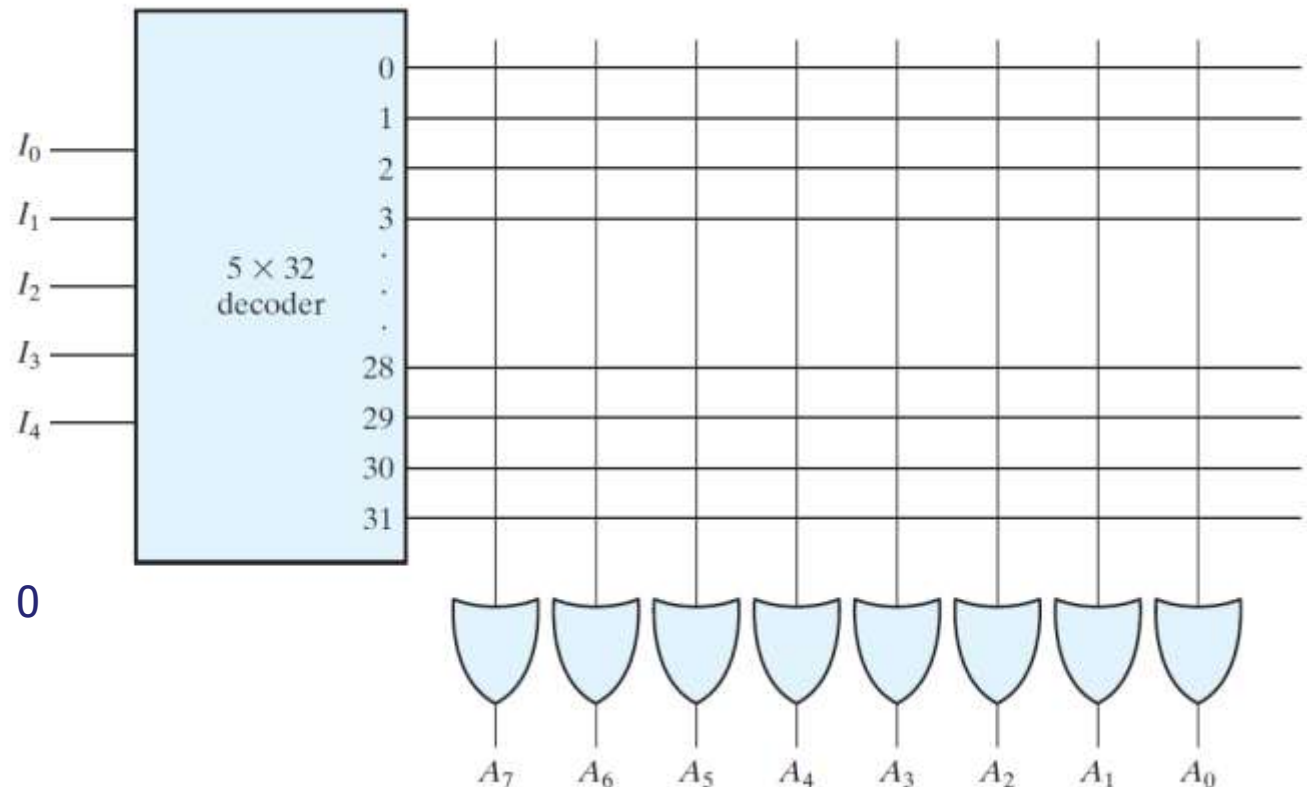- 32×8 ROM with 256 intersections:
 - No connection = 0
 - Connection = 1





ROM Example


Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0

- Example of "programmed" ROM:

- "x" indicates connection

- Programming of ROM

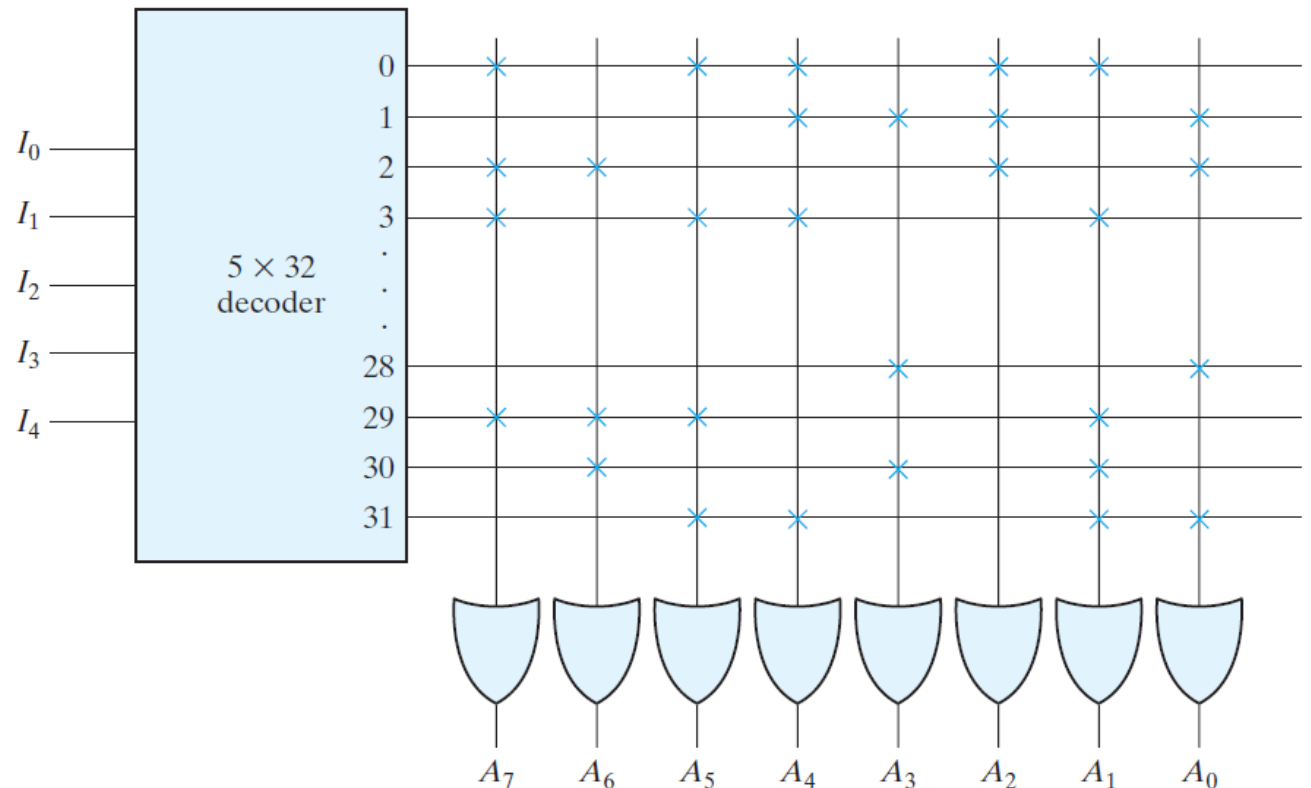- Connections implemented as "fuses" (logic 1)
- Blown fuse (open) indicates 0
- Higher voltage can blow fuse





Types of ROM

- Mask Programmed ROM
 - During fabrication of ROM
 - Only economical in large quantities
- Programmable ROM (PROM)
 - ROM with all fuses intact
 - High-voltage pulse on special pin can irreversibly blow fuses
 - *Note:* hardware procedure despite "programmable"
- Erasable PROM (EPROM)
 - Connections can be restored
 - Exposure to UV light resets EPROM
- Electrically-erasable PROM (EEPROM)
 - Electric signal can reset connections (no UV required)





Implementing Functions using PROM

- The shown PROM implements the following two Boolean functions:

- $F1(x,y,z)$

$$= \sum(0,3,5,6)$$

$$= x'y'z' + x'yz$$

$$+ xy'z + xyz'$$

- $F2(x,y,z)$

$$= \sum(0,1,2,4,7)$$

$$= x'y'z' + x'y'z$$

$$+ x'yz' + xy'z' + xyz$$

