



COE211: Digital Logic Design

Introduction



Digital Computer Systems

- Digital systems consider *discrete* amounts of data
- **Examples**
 - 26 letters in the alphabet
 - 10 decimal digits
- **Larger quantities can be built from discrete values:**
 - Words made of letters
 - Numbers made of decimal digits (e.g. 239875.32)
- **Computers operate on binary values (0 and 1)**
- **Easy to represent binary values electrically**
 - Voltages and currents
 - Can be implemented using circuits
 - Create the building blocks of modern computers



Understanding Decimal Numbers

- **Decimal numbers are made of decimal digits: (0,1,2,3,4,5,6,7,8,9) \Rightarrow Base = 10**
- **But how many items does a decimal number represent?**
 - $8653 = 8 \times 10^3 + 6 \times 10^2 + 5 \times 10^1 + 3 \times 10^0$
 - $\text{Number} = d_3 \times B^3 + d_2 \times B^2 + d_1 \times B^1 + d_0 \times B^0 = \text{Value}$
- **What about fractions?**
 - $97654.35 = 9 \times 10^4 + 7 \times 10^3 + 6 \times 10^2 + 5 \times 10^1 + 4 \times 10^0 + 3 \times 10^{-1} + 5 \times 10^{-2}$
 - In formal notation $\rightarrow (97654.35)_{10}$



Understanding Binary Numbers

- Binary numbers are made of **binary digits (bits)**:
 - 0 and 1
- How many items does a binary number represent?
 - $\quad\quad\quad 8 \quad 4 \quad 2 \quad 1 = \text{Weights}$
 - $(1011)_2 = 1 \times 2^3 + 0 \times 2^2 + 1 \times 2^1 + 1 \times 2^0 = (11)_{10}$
- What about fractions?
 - $(110.10)_2 = 1 \times 2^2 + 1 \times 2^1 + 0 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2}$
- Groups of eight bits are called a byte
 - $(11001001)_2$
- Groups of four bits are called a nibble
 - $(1101)_2$



Understanding Octal Numbers

- Octal numbers are made of octal digits: (0,1,2,3,4,5,6,7)
- How many items does an octal number represent?
 - $512 \quad 64 \quad 8 \quad 1 = \text{Weights}$
 - $(4536)_8 = 4 \times 8^3 + 5 \times 8^2 + 3 \times 8^1 + 6 \times 8^0 = (1362)_{10}$
- What about fractions?
 - $(465.27)_8 = 4 \times 8^2 + 6 \times 8^1 + 5 \times 8^0 + 2 \times 8^{-1} + 7 \times 8^{-2}$
- Octal numbers don't use digits 8 or 9



Understanding Hexadecimal Numbers

- **Hexadecimal numbers are made of 16 digits:**
 - (0,1,2,3,4,5,6,7,8,9,A, B, C, D, E, F)
- **How many items does a hex number represent?**
 - $4096 \quad 256 \quad 16 \quad 1 = \text{Weights}$
 - $(3A9F)_{16} = 3 \times 16^3 + 10 \times 16^2 + 9 \times 16^1 + 15 \times 16^0 = 14999_{10}$
- **What about fractions?**
 - $(2D3.5)_{16} = 2 \times 16^2 + 13 \times 16^1 + 3 \times 16^0 + 5 \times 16^{-1} = 723.3125_{10}$
- **Note that each hexadecimal digit can be represented with four bits**
 - $(1110)_2 = (E)_{16}$



Why Use Binary Numbers?

- Easy to represent 0 and 1 using electrical values
- Possible to tolerate noise
- Easy to transmit data
- Easy to build binary circuits


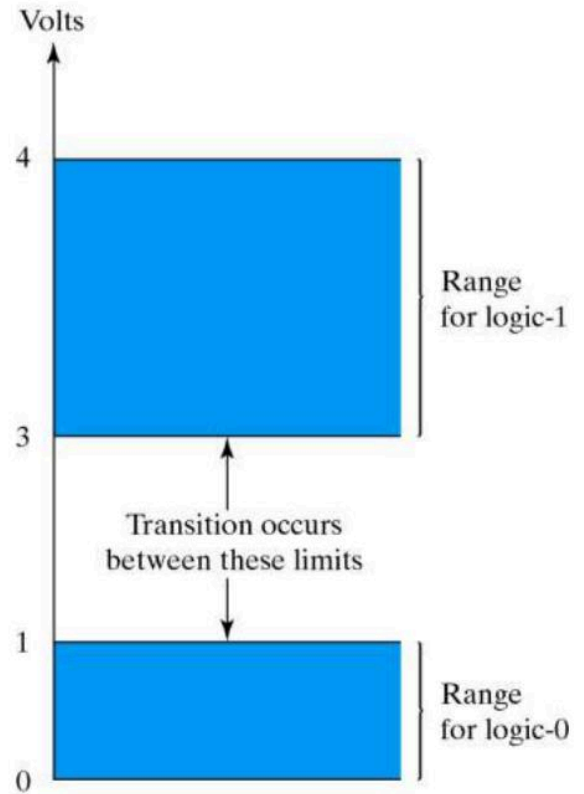


Fig. 1-3 Example of binary signals

 

Convert an Integer *from* Decimal *to* Another Base

For each digit position:

1. Divide decimal number by the base (e.g. 2)
2. The *remainder* is the lowest-order digit
3. Repeat first two steps until no *divisor* remains

Example for $(13)_{10}$:

	Quotient	Remainder	Coefficient
$13/2 =$	6	, 1	$a_0 = 1$
$6/2 =$	3	, 0	$a_1 = 0$
$3/2 =$	1	, 1	$a_2 = 1$
$1/2 =$	0	, 1	$a_3 = 1$

$$\text{Answer } (13)_{10} = (a_3 a_2 a_1 a_0)_2 = (1101)_2$$

MSB

LSB



Convert a Fraction *from* Decimal *to* Another Base

For each digit position:

1. Multiply decimal number by the base (e.g. 2)
2. The *integer* is the highest-order digit
3. Repeat first two steps until fraction becomes zero

Example for $(0.625)_{10}$:

	Integer		Fraction	Coefficient
$0.625 \times 2 =$	1	+	0.250	$a_{-1} = 1$
$0.250 \times 2 =$	0	+	0.500	$a_{-2} = 0$
$0.500 \times 2 =$	1	+	0	$a_{-3} = 1$

$$\text{Answer } (0.625)_{10} = (0.a_{-1} a_{-2} a_{-3})_2 = (0.101)_2$$

↑
MSB

↑
LSB



Conversion Between Base 16 and Base 2

- **Conversion is easy!**
 - Determine the 4-bit value for each hex digit**
- **Note that there are 16 different values of four bits**
- **Easier to read and write in hexadecimal**
- **Representations are equivalent!**

$$3A9F_{16} = \begin{array}{cccc} \underline{0011} & \underline{1010} & \underline{1001} & \underline{1111} \\ 3 & A & 9 & F \end{array}_2$$



The Growth of Binary Numbers

n	2^n
0	$2^0=1$
1	$2^1=2$
2	$2^2=4$
3	$2^3=8$
4	$2^4=16$
5	$2^5=32$
6	$2^6=64$
7	$2^7=128$



n	2^n
8	$2^8=256$
9	$2^9=512$
10	$2^{10}=1024$
11	$2^{11}=2048$
12	$2^{12}=4096$
20	$2^{20}=1M$
30	$2^{30}=1G$
40	$2^{40}=1T$

Kilo

Mega

Giga

Tera



Understanding Binary Coded Decimal

- **Binary Coded Decimal (BCD)** represents each decimal digit with four bits

Ex. $\underline{0011} \ \underline{0010} \ \underline{1001} = 329_{10}$
 3 2 9

- This is NOT the same as $001100101001_2 = 809_{10}$

Digit	BCD Code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001



Putting It All Together

Decimal	Binary	Octal	Hexadecimal	BCD
0	0000	0	0	000
1	0001	1	1	0001
2	0010	2	2	0010
3	0011	3	3	0011
4	0100	4	4	0100
5	0101	5	5	0101
6	0110	6	6	0110
7	0111	7	7	0111
8	1000	10	8	1000
9	1001	11	9	1001
10	1010	12	A	0001 0000
11	1011	13	B	0001 0001
12	1100	14	C	0001 0010
13	1101	15	D	0001 0011
14	1110	16	E	0001 0100
15	1111	17	F	0001 0101



How To Represent Signed Numbers

- Plus and minus signs are used for decimal numbers:
 - 25 (or +25), -16, etc
- In computers, everything is represented as *bits*
- Three types of signed binary number representations:
 - signed magnitude
 - 1's complement
 - 2's complement
- In each case: left-most bit indicates the sign: '0' for positive and '1' for negative



Signed Magnitude Representation

- The left most bit is designated as the *sign* bit while the remaining bits form the *magnitude*

$$\begin{array}{ccc} & \text{00001100}_2 = 12_{10} & \\ \swarrow & & \nwarrow \\ \text{Sign bit} & & \text{Magnitude} \end{array}$$

$$\begin{array}{ccc} & \text{10001100}_2 = -12_{10} & \\ \swarrow & & \nwarrow \\ \text{Sign bit} & & \text{Magnitude} \end{array}$$



One's Complement Representation

- The one's complement of a binary number is done by complementing (i.e. inverting) all bits

1's comp of **00110011** is **11001100**

1's comp of **10101010** is **01010101**

- For a n -bit number N the 1's complement is $(2^n - 1) - N$
- Called "*diminished radix complement*" by Mano
- To find the negative of a 1's complement number take its 1's complement





One's Complement Representation

4 bits
↓
16 combinations

7	0111
6	0110
.	.
.	.
1	0001
0	0000
- 0	1111
- 1	1110
.	.
.	.
- 6	1001
- 7	1000



Two's Complement Representation

- The two's complement of a binary number is done by complementing (inverting) all bits then adding 1
 - 2's comp of **00110011** is **11001101**
 - 2's comp of **10101010** is **01010110**
- For an n -bit number N the 2's complement is $(2^n - 1) - N + 1$
- Called "*radix complement*" by Mano
- To find the negative of a 2's complement number take its 2's complement

$$\begin{array}{c} \text{00001100}_2 = 12_{10} \\ \swarrow \quad \searrow \\ \text{Sign bit} \quad \text{Magnitude} \end{array}$$

$$\begin{array}{c} \text{11110100}_2 = -12_{10} \\ \swarrow \quad \searrow \\ \text{Sign bit} \quad \text{Code} \end{array}$$



Two's Complement Shortcuts

- **Algorithm 1:** Complement each bit then add 1 to the result

$$\begin{array}{r} N = 01100101 \\ \quad 10011010 \\ + \quad \quad \quad 1 \\ \hline 10011011 \end{array} \quad \nearrow \quad \begin{array}{r} [N] = 10011011 \\ \quad 01100100 \\ + \quad \quad \quad 1 \\ \hline 01100101 \end{array}$$

- **Algorithm 2:** Starting with the least significant bit, copy all of the bits up to and including the first '1' bit, then complement the remaining bits

$$\begin{array}{r} N = 01100110 \\ [N] = 10011010 \end{array}$$



Two's Complement Representation

4 bits
↓
16 combinations

7	0111
6	0110
.	.
2	0010
1	0001
0	0000
- 1	1111
- 2	1110
.	.
.	.
- 7	1001
- 8	1000



Putting All Together

Decimal	Signed-2's Complement	Signed-1's Complement	Signed Magnitude
+7	0111	0111	0111
+6	0110	0110	0110
+5	0101	0101	0101
+4	0100	0100	0100
+3	0011	0011	0011
+2	0010	0010	0010
+1	0001	0001	0001
+0	0000	0000	0000
-0	—	1111	1000
-1	1111	1110	1001
-2	1110	1101	1010
-3	1101	1100	1011
-4	1100	1011	1100
-5	1011	1010	1101
-6	1010	1001	1110
-7	1001	1000	1111
-8	1000	—	—



Finite-Precision Number Representation

- Machines that use 2's complement arithmetic can represent integers in the range

$$-2^{n-1} \leq N \leq 2^{n-1} - 1$$

n is the number of bits used for representing **N**

Note that $2^{n-1} - 1 = (011..11)_2$ and $-2^{n-1} = (100..00)_2$

- 2's complement code has more negative numbers than positive
- 1's complement code has 2 representations for zero
- For an **n**-bit number in base (i.e. radix) **z** there are z^n different unsigned values (combinations)

$$(0, 1, \dots, z^{n-1})$$



2's Complement Addition

- Using 2's complement representation, adding numbers is easy

Step 1: Add binary numbers

Step 2: Ignore the resulting carry bit

- For example: $(12)_{10} + (1)_{10}$

$$(12)_{10} = +(1100)_2 \\ = 01100_2 \text{ in 2's comp.}$$

$$(1)_{10} = +(0001)_2 \\ = 00001_2 \text{ in 2's comp.}$$

			0	1	1	0	0	
Add	+		0	0	0	0	1	

Final Result		0	0	1	1	0	1	
		↑						
		Ignore						



2's Complement Subtraction

- Using 2's complement representation, subtracting numbers is also easy

Step 1: Take 2's complement of 2nd operand


Step 2: Add binary numbers

Step 3: Ignore the resulting carry bit

- For example: $(12)_{10} - (1)_{10}$

$$\begin{aligned} (12)_{10} &= +(1100)_2 \\ &= 01100_2 \text{ in 2's comp.} \end{aligned}$$
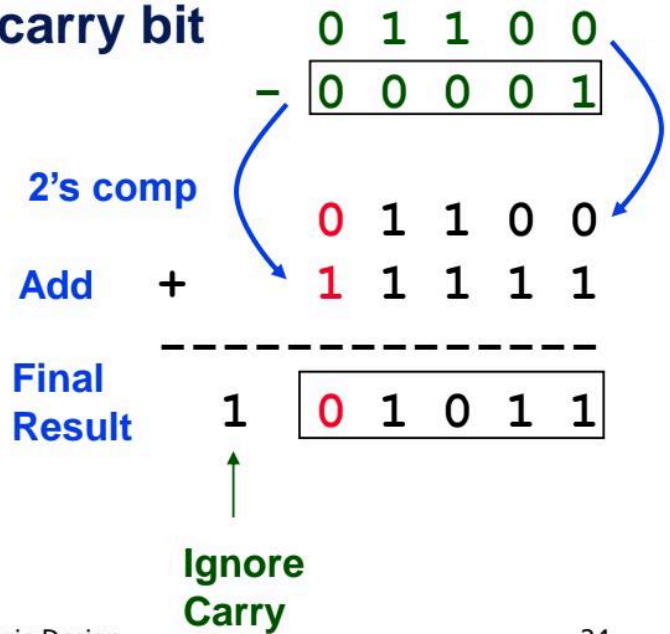
$$\begin{aligned} (-1)_{10} &= -(0001)_2 \\ &= 11111_2 \text{ in 2's comp.} \end{aligned}$$





2's Complement Subtraction (Cont'd)

- **Example 2: $(13)_{10} - (5)_{10}$**
 $(13)_{10} = +(1101)_2 = (01101)_2$
 $(-5)_{10} = -(0101)_2 = (11011)_2$
- **Adding these two 5-bit codes:**

$$\begin{array}{r} 01101 \\ + 11011 \\ \hline \end{array}$$

Carry \longrightarrow $\boxed{1}01000$

- **Discarding the carry bit, the sign bit is seen to be zero, indicating a positive result**

Indeed: $(01000)_2 = +(8)_{10}$



2's Complement Subtraction (Cont'd)

- **Example 3: $(5)_{10} - (12)_{10}$**
 $(5)_{10} = +(0101)_2 = (00101)_2$
 $(-12)_{10} = -(1100)_2 = (10100)_2$
- **Adding these two 5-bit codes:**

$$\begin{array}{r} 00101 \\ + 10100 \\ \hline \end{array}$$

Carry \longrightarrow 0 11001

- **Here, there is no carry bit and the sign bit is 1. This indicates a negative result, which is what we expect: $(11001)_2 = -(7)_{10}$**



Gray Code

- **Gray code is not a number system**
It is an alternate way to represent four bit data
- **Only one bit changes from one decimal digit to the next**
- **Useful for reducing errors in communication**
- **Can be scaled to larger numbers**

Digit	Binary	Gray Code
0	0000	0000
1	0001	0001
2	0010	0011
3	0011	0010
4	0100	0110
5	0101	0111
6	0110	0101
7	0111	0100
8	1000	1100
9	1001	1101
10	1010	1111
11	1011	1110
12	1100	1010
13	1101	1011
14	1110	1001
15	1111	1000



Text: ASCII Characters

- ASCII: Maps 128 characters to 7-bit code.
 - both printable and non-printable (ESC, DEL, ...) characters
<http://www.asciitable.com/>

00 nul	10 dle	20 sp	30 0	40 @	50 P	60 `	70 p
01 soh	11 dc1	21 !	31 1	41 A	51 Q	61 a	71 q
02 stx	12 dc2	22 "	32 2	42 B	52 R	62 b	72 r
03 etx	13 dc3	23 #	33 3	43 C	53 S	63 c	73 s
04 eot	14 dc4	24 \$	34 4	44 D	54 T	64 d	74 t
05 enq	15 nak	25 %	35 5	45 E	55 U	65 e	75 u
06 ack	16 syn	26 &	36 6	46 F	56 V	66 f	76 v
07 bel	17 etb	27 '	37 7	47 G	57 W	67 g	77 w
08 bs	18 can	28 (38 8	48 H	58 X	68 h	78 x
09 ht	19 em	29)	39 9	49 I	59 Y	69 i	79 y
0a nl	1a sub	2a *	3a :	4a J	5a Z	6a j	7a z
0b vt	1b esc	2b +	3b ;	4b K	5b [6b k	7b {
0c np	1c fs	2c ,	3c <	4c L	5c \	6c l	7c
0d cr	1d gs	2d -	3d =	4d M	5d]	6d m	7d }
0e so	1e rs	2e .	3e >	4e N	5e ^	6e n	7e ~
0f si	1f us	2f /	3f ?	4f O	5f _	6f o	7f del




COE211: Digital Logic Design

Boolean Algebra and Logic Gates



Describing Circuit Functionality: Inverter

 - Basic logic functions have symbols
- The same functionality can be represented with a **truth table**
 - Truth table completely specifies outputs for all input combinations
- This is an inverter
 - An input of **0** is inverted to a **1**
 - An input of **1** is inverted to a **0**



Truth Table

A	Y
0	1
1	0

Input Output




The AND Gate

- This is an **AND** gate
- If the two input signals are **asserted** (i.e. high) the output will also be asserted. Otherwise, the output will be **deasserted** (i.e. low)

Truth Table

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

 




The OR Gate

- This is an **OR** gate
- If either of the two input signals is **asserted**, or both of them are, the output will be **asserted**

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

 



The NAND Gate

- The **NAND** gate is a combination of an **AND** gate followed by an inverter
 - $\text{NAND}(A, B) \rightarrow (A \text{ AND } B)'$



$$Y = \overline{A \cdot B}$$


A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0




The Universal Property of NAND

- You can implement any function using: NOT, AND, and OR. They represent a **logically complete** set.
- You can use only NAND gates to implement the above three gates. Therefore, NAND alone is a **logically complete** set.


NOT

 

AND

 

OR

 



The NOR Gate

- A **NOR** gate is a combination of an **OR** gate followed by an inverter
 - $\text{NOR}(A, B) \rightarrow (A+B)'$






$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0



The Universal Property of NOR

   
- Similarly, you can use only NOR gates to implement NOT, AND, and OR. Therefore, NOR alone is a **logically complete** set.







Exclusive-OR and Exclusive-NOR Circuits

 Exclusive-OR (XOR) produces a HIGH output whenever the two inputs are at opposite levels



A	B	x
0	0	0
0	1	1
1	0	1
1	1	0


XOR gate symbols

  





Exclusive-NOR Circuits

 Exclusive-NOR (XNOR) produces a HIGH output whenever the two inputs are at the same level




XNOR gate symbols

  




XOR Function

 XOR function can also be implemented with AND/OR gates (also NANDs)



(a) With AND-OR-NOT gates

 

(b) With NAND gates

Fig. 3-32 Exclusive-OR Implementations



XOR Function

- Even function – even number of inputs are 1
- Odd function – odd number of inputs are 1

A	BC		B	
	00	01	11	10
0		1		1
1	1		1	

(a) Odd function
 $F = A \oplus B \oplus C$

A	BC		B	
	00	01	11	10
0	1		1	
1		1		1


(a) Even function
 $F = (A \oplus B \oplus C)'$

Fig. 3-33 Map for a Three-variable Exclusive-OR Function



Describing Circuit Functionality: Waveforms

 - Waveforms provide another approach for representing functionality
- Values are either high (logic 1) or low (logic 0)
- Can you create a truth table from the waveforms?




AND Gate

x	y	f
0	0	0
0	1	0
1	0	0
1	1	1





Consider Three-input Gates

3 Input OR Gate

 

A	B	C	$x = A + B + C$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

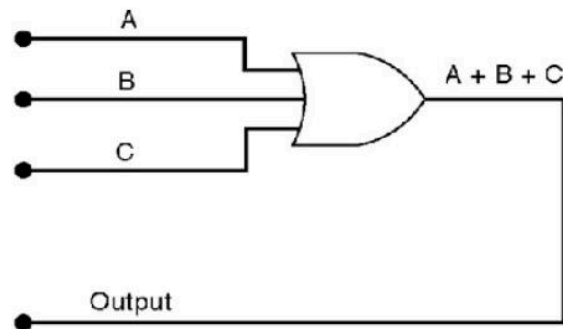 



Boolean Algebra

- Useful for identifying and *minimizing* circuit functionality
- Identity elements
 - $a + 0 = a$
 - $a \cdot 1 = a$
 - **0** is the identity element for the **+** operation
 - **1** is the identity element for the **•** operation
- The Complement: for every element 'a', there exists a unique element called a' (or \bar{a}) (complement of a) such that :
 - $a + a' = 1$
 - $a \cdot a' = 0$



George Boole (1815 - 1864)


- Father of Boolean algebra
- Boole's system (*detailed in his 'An Investigation of the Laws of Thought, on Which Are Founded the Mathematical Theories of Logic and Probabilities', 1854*) was based on a binary approach, processing only two objects - the yes-no, true-false, on-off, zero-one approach.
- Surprisingly, given his standing in the academic community, Boole's idea was either criticized or completely ignored by the majority of his peers.
- Eventually, one bright student, **Claude Shannon** (1916-2001), picked up the idea and ran with it.



Laws of Boolean Algebra


- Commutative Law of ORing:

$$A + B = B + A$$

 

- Commutative Law of ANDing:

$$A \cdot B = B \cdot A$$

 




Laws of Boolean Algebra (Cont'd)


- Associative Law of ORing:

$$A + (B + C) = (A + B) + C$$

 

- Associative Law of ANDing:
 
$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$






Laws of Boolean Algebra (Cont'd)

■ Distributive Law:

- *Note:* To simplify notation, the \cdot operator is frequently omitted. When two elements are written next to each other, the **AND** (\cdot) operator is implied

$$\mathbf{A(B + C) = AB + AC}$$

 



Rules of Boolean Algebra

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

$$10. A + AB = A$$


$$11. A + \bar{A}B = A + B$$

$$12. (A + B)(A + C) = A + BC$$



Rules of Boolean Algebra Cont'd


■ Rule 1

 

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

■ Rule 2

 


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table



Rules of Boolean Algebra Cont'd


■ Rule 3

 

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

■ Rule 4

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table



Rules of Boolean Algebra Cont'd


■ Rule 5

 

A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table

■ Rule 6

 


A	B	X
0	0	0
0	1	1
1	0	1
1	1	1

OR Truth Table



Rules of Boolean Algebra Cont'd


■ Rule 7

 

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table

■ Rule 8

 


A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

AND Truth Table



Rules of Boolean Algebra Cont'd

■ Rule 9

 

■ Rule 10 (the absorption rule): $A + AB = A$

A	B	AB	$A + AB$
0	0	0	0
0	1	0	0
1	0	0	1
1	1	1	1

↑ equal ↑



Rules of Boolean Algebra Cont'd

- Rule 11: $A + \overline{A}B = A + B$

A	B	$\overline{A}B$	$A + \overline{A}B$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

- Rule 12: $(A + B)(A + C) = A + BC$

A	B	C	$A + B$	$A + C$	$(A + B)(A + C)$	BC	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1


↑ equal ↑



De Morgan's Theorems

(by Augustus De Morgan (1806 - 1871), an English mathematician and logician)
 
$$\overline{A \cdot B} = \overline{A} + \overline{B}$$



$$\overline{A + B} = \overline{A} \cdot \overline{B}$$



General:

$$\overline{A \cdot B \cdot C \cdot D} = \overline{A} + \overline{B} + \overline{C} + \overline{D}$$

$$\overline{A + B + C + D} = \overline{A} \cdot \overline{B} \cdot \overline{C} \cdot \overline{D}$$



De Morgan's Theorems Example

$$\overline{(A.B + C) (A + B.C)} =$$

$$\overline{(A.B + C)} + \overline{(A + B.C)} =$$

$$(\overline{A.B.C}) + (\overline{A.B.C}) =$$


$$(\overline{A} + \overline{B}).\overline{C} + \overline{A}.\overline{(B + C)} =$$

$$\overline{A}.\overline{C} + \overline{B}.\overline{C} + \overline{A}.\overline{B} + \overline{A}.\overline{C} =$$

$$\overline{A}.\overline{C} + \overline{B}.\overline{C} + \overline{A}.\overline{B}$$

Converting AND to OR

 - Using De Morgan's Theorems, AND can be converted to OR (with some help from NOT)
- Consider the following gate:



A	B	\overline{A}	\overline{B}	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$
0	0	1	1	1	0
0	1	1	0	0	1
1	0	0	1	0	1
1	1	0	0	0	1

Same as $A+B$

*To convert AND to OR
(or vice versa),
invert inputs and output.*



Standard Forms of Boolean Expressions

- The sum-of-product (SOP) form

$$\text{Example: } X = AB + CD + EF$$

- The product of sum (POS) form


$$\text{Example: } X = (A + B)(C + D)(E + F)$$



Sum-of-Products Expression

- A *literal* is a variable or the complement of a variable.
Examples: x, y, \bar{x}, \bar{y}
- A *product term* is a single literal or a logical product of two or more literals. Examples: $\bar{z}, w.x.y, x.\bar{y}.z, \bar{w}.\bar{y}.z$
- A *sum-of-products* (SOP) expression is a logical sum of product terms.
Example: $\bar{z} + w.x.y + x.\bar{y}.z + \bar{w}.\bar{y}.z$

 
- Every SOP expression can be realized by a two-level circuit containing AND gates followed by an OR gate





SOP With NANDs

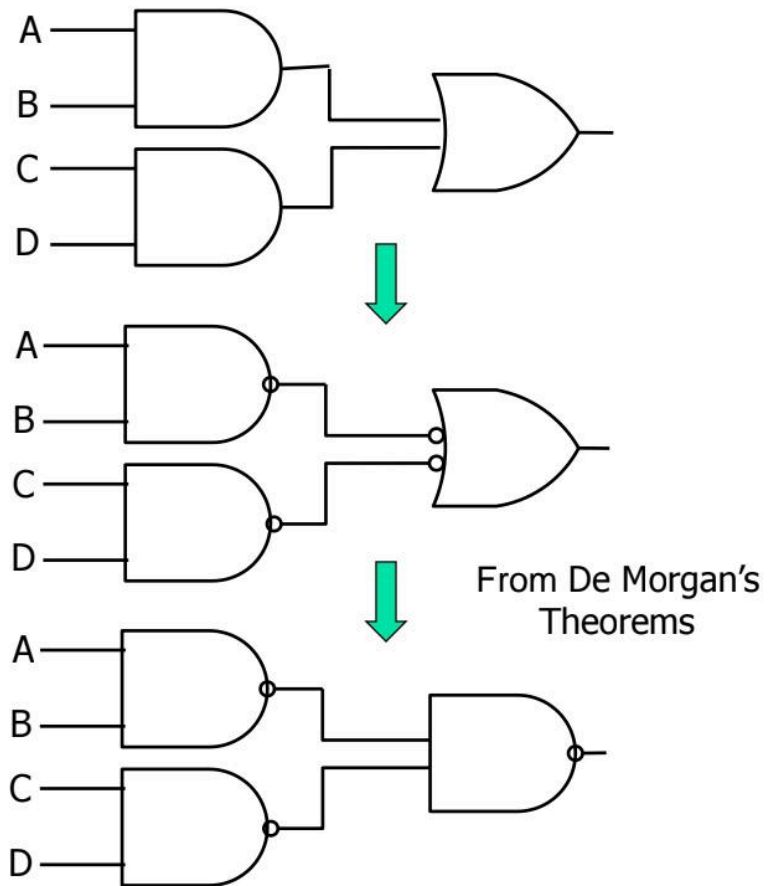
- A SOP expression can be implemented with only NAND gates:





Function Representation Conversion

 - Need to transit between a Boolean expression, a truth table, and a circuit (symbols)
- All three formats are equivalent





Minterm

- For each truth-table row a product term can be defined that evaluates to 1 only when the inputs have the values listed in that row.
- If the product term contains each input variable exactly once it is called a **minterm**

Row	A	B	C	Minterm
0	0	0	0	$\bar{A}.\bar{B}.\bar{C}$
1	0	0	1	$\bar{A}.\bar{B}.C$
2	0	1	0	$\bar{A}.B.\bar{C}$
3	0	1	1	$\bar{A}.B.C$
4	1	0	0	$A.\bar{B}.\bar{C}$
5	1	0	1	$A.\bar{B}.C$
6	1	1	0	$A.B.\bar{C}$
7	1	1	1	$A.B.C$



From Truth Table to Boolean Expression

- Any logic function can be expressed algebraically by taking the **OR** of all those **minterms** corresponding to the truth-table rows for which the function produces a 1 output.
- Example:* Majority detector.

Row	A	B	C	Minterm	R
0	0	0	0	$\bar{A}.\bar{B}.\bar{C}$	0
1	0	0	1	$\bar{A}.\bar{B}.C$	0
2	0	1	0	$\bar{A}.B.\bar{C}$	0
3	0	1	1	$\bar{A}.B.C$	1
4	1	0	0	$A.\bar{B}.\bar{C}$	0
5	1	0	1	$A.\bar{B}.C$	1
6	1	1	0	$A.B.\bar{C}$	1
7	1	1	1	$A.B.C$	1

$$R = \bar{A}.B.C + A.\bar{B}.C + A.B.\bar{C} + A.B.C$$

- Alternate forms:

$$R = m_3 + m_5 + m_6 + m_7$$


$$R = \Sigma (3, 5, 6, 7)$$



Converting to a Circuit

- Number of 1's in truth table output column equals AND terms for Sum-of-Products (SOP)

x	y	z	G
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 

$$G = xyz + xyz' + x'yz$$



Canonical Form of a Function

- A form is *canonical* if representation of a function in this form is unique.
- Examples:
 - Truth table representation of a function.
 - Sum of minterms representation of a function.



Boolean vs. Ordinary Algebra

■ Differences

- Distributivity of + over • holds for Boolean, but not for ordinary algebra

$$x+(y \cdot z) = (x+y) \cdot (x+z)$$

- Boolean algebra does not have inverse elements for + or •

Thus, no subtraction or division operators

- Complement is not defined in ordinary algebra



COE211: Digital Logic Design

Simplification of Boolean Functions



Overview

- Introduction to Karnaugh Maps
- Karnaugh Maps Rules and Methods
- Two and Three-Variable K-Maps
- Four-Variable K-Maps
- Simplification Techniques
- Don't Cares Conditions



Karnaugh Maps

- Alternate way of representing Boolean functions
 - Each row in the truth table is represented by a square
 - Each square represents a *minterm*
- Easy to convert between truth table, K-map, and SOP
 - Un-optimized form: number of 1's in K-map equals number of minterms (products) in SOP
 - Optimized form: reduced number of minterms

		<u>y</u>	
		0	1
x	0	$x'y'$	$x'y$
	1	xy'	xy

$$F = \Sigma(m_0, m_1) = x'y + x'y'$$

		<u>y</u>	
		0	1
x	0	1	1
	1	0	0

x	y	F
0	0	1
0	1	1
1	0	0
1	1	0



Karnaugh Maps (cont'd)

- A Karnaugh map is a graphical tool for assisting in the general simplification procedure
- Two variable maps

		<i>B</i>	
		0	1
<i>A</i>	0	0	1
	1	1	0

$$F = A\bar{B} + \bar{A}B$$

		<i>B</i>	
		0	1
<i>A</i>	0	0	1
	1	1	1

$$F = AB + \bar{A}B + A\bar{B}$$

- Three variable maps

		<i>BC</i>			
		00	01	11	10
<i>A</i>	0	0	1	0	1
	1	1	1	1	1

<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$



Rules for K-Maps

- We can reduce functions by **circling** 1's in the K-map
- Each circle represents minterm reduction
- After circling, deduce a minimized AND-OR form

Rules to consider

- Every cell containing a 1 must be included at least once
- The largest possible "power of 2 rectangle" should be used
- Use the smallest possible number of rectangles



Karnaugh Maps Examples

- Two variable maps

	B	0	1	
A	0	0	1	$F = A\bar{B} + \bar{A}B$
	1	1	0	

	B	0	1	
A	0	0	1	$F = AB + \bar{A}B + A\bar{B}$ $F = A + B$
	1	1	1	

- Three variable maps


	BC	00	01	11	10	
A	0	0	1	0	1	$F = A + \bar{B}C + B\bar{C}$
	1	1	1	1	1	

$$F = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + A\bar{B}C + AB\bar{C} + ABC$$




Karnaugh Maps Examples (cont'd)

FIGURE 3.4 Map for Example 3.1, $F(x, y, z) = \Sigma(2, 3, 4, 5) = x'y + xy'$

 

Copyright © 2013 Pearson Education, publishing as Prentice Hall

FIGURE 3.6 Map for Example 3.3, $F(x, y, z) = \Sigma(0, 2, 4, 5, 6) = z' + xy'$

 

Note: $y'z' + yz' = z'$

Copyright © 2013 Pearson Education, publishing as Prentice Hall



Karnaugh Maps Examples (cont'd)

	b	0	1
a	0	0	1
1	0	0	1

$$f = b$$

	b	0	1
a	0	1	1
1	0	0	0

$$g = a'$$

	bc	00	01	11	10
a	0	0	0	1	0
1	0	1	1	1	1

$$\text{cout} = bc + ac + ab$$

	bc	00	01	11	10
a	0	0	0	1	1
1	0	0	1	1	1

$$f = b$$

1. Circle the largest groups possible
2. Group dimensions must be a power of 2
3. Remember what circling means!



K-Maps of 3-variable XOR Function

- Odd function – odd number of inputs are 1
- Even function – even number of inputs are 1

A	BC		B	
	00	01	11	10
0		1		1
1	1		1	

(a) Odd function
 $F = A \oplus B \oplus C$


A	BC		B	
	00	01	11	10
0	1		1	
1		1		1

(a) Even function
 $F = (A \oplus B \oplus C)'$

Fig. 3-33 Map for a Three-variable Exclusive-OR Function



Example using 1-bit Adder

 

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

How to use a Karnaugh Map instead of the Algebraic simplification?

$$S = A'B'Cin + A'BCin' + A'BCin + ABCin$$

$$Cout = A'BCin + A B'Cin + ABCin' + ABCin$$

$$= A'BCin + ABCin + AB'Cin + ABCin + ABCin' + ABCin$$


$$= (A' + A)BCin + (B' + B)ACin + (Cin' + Cin)AB$$

$$= 1 \cdot BCin + 1 \cdot ACin + 1 \cdot AB$$


$$= BCin + ACin + AB$$



Example using 1-bit Adder (cont'd)

 

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Karnaugh Map for Cout


Now we have to cover all the 1s in the Karnaugh Map using the largest rectangles and as few rectangles as we can.



Example using 1-bit Adder (cont'd)

 

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 


Karnaugh Map for Cout

Now we have to cover all the 1s in the Karnaugh Map using the largest rectangles and as few rectangles as we can.

$$Cout = BCin + AB + ACin$$




Example using 1-bit Adder (cont'd)

 

Can you draw the circuit diagrams?

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Karnaugh Map for S

$$S = A \bar{B} \bar{Cin} + \bar{A} \bar{B} Cin + ABCin + \bar{A} B \bar{Cin}$$

No Possible Reduction!



Karnaugh Maps for 4-Input Functions

- Represent functions of 4 inputs with 16 minterms
- Use same rules developed for 3-input functions


 


Fig. 3-8 Four-variable Map

 

Karnaugh Map: 4-Variable Example

$$F(A,B,C,D) = \Sigma m(0, 2, 3, 5, 6, 7, 8, 10, 11, 14, 15)$$



$$F = C + A'BD + B'D'$$



Design Examples

		c			
		00	01	11	10
A	00	0	1	1	1
	01	0	0	1	1
	11	0	0	0	0
	10	0	0	1	0

K-map for LT

		c			
		00	01	11	10
A	00	1	0	0	0
	01	0	1	0	0
	11	0	0	1	0
	10	0	0	0	1

K-map for EQ

		c			
		00	01	11	10
A	00	0	0	0	0
	01	1	0	0	0
	11	1	1	0	1
	10	1	1	0	0

K-map for GT

$$LT = A' C + A' B' D + B' C D$$

$$EQ = A' B' C' D' + A' B C' D + A B C D + A B' C D'$$


$$GT = A C' + B C' D' + A B D'$$

Can you draw the truth table for these examples?



Physical Implementation

A B C D

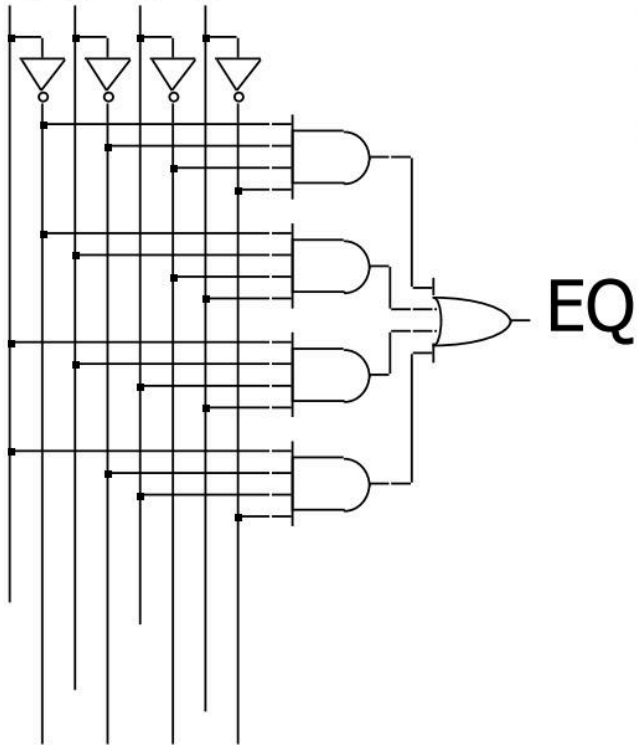

Step 1: Truth table

Step 2: K-map

Step 3: Minimized sum-of-products

Step 4: Physical implementation with gates

		C		
	1	0	0	0
	0	1	0	0
A	0	0	1	0
	0	0	0	1
		D		

K-map for EQ



Karnaugh Maps: Don't Cares

- In some cases, outputs are undefined
- We "don't care" if the circuit produces a '0' or a '1'
- This knowledge can be used to simplify functions

CD		AB		A	
		00	01	11	10
C	00	0	0	X	0
	01	1	1	X	1
	11	1	1	0	0
	10	0	X	0	0

- Treat X's like either 1's or 0's
- Very useful
- OK to leave some X's uncovered



Don't Care Conditions

- In some situations, we don't care about the value of a function for certain combinations of the variables
 - these combinations may be impossible in certain contexts
 - or the value of the function may not matter when the combinations occur
- In such situations we say the function is incompletely specified and there are multiple (completely specified) logic functions that can be used in the design
 - so we can select a function that gives the simplest circuit
- When constructing the terms in the simplification procedure, we can choose to either cover or not cover the don't care conditions



Don't Cares Examples

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	x	x	x	1
	11	1	1	1	x
	10	x	0	1	1

$$F = A'C'D + B + AC$$

Alternative covering:

		CD			
		00	01	11	10
AB	00	0	1	0	0
	01	x	x	x	1
	11	1	1	1	x
	10	x	0	1	1

$$F = A'B'C'D + ABC' + BC + AC$$



Don't Cares Examples (cont'd)

$$f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$$

- $f = A'D + B'C'D$

without don't cares

- $f = A'D + C'D$

with don't cares

		C		
	0	1	1	0
	0	1	1	X
A	X	X	0	0
	0	1	0	0
		D		

by using don't care as a "1"
a 2-cube can be formed
rather than a 1-cube to cover
this node

don't cares can be treated as
1s or 0s
depending on which is more
advantageous



Definition of Terms

- **Implicant**
 - Single product term of the ON-set (terms that create a logic 1)
- **Prime implicant**
 - Implicant that can't be combined with another to form an implicant with fewer literals
- **Essential prime implicant**
 - Prime implicant is essential if it alone covers a minterm in the K-map
 - Remember that all squares marked with 1 must be covered
- **Objective:**
 - Grow implicants into prime implicants (minimize literals per term)
 - Cover the K-map with as few prime implicants as possible (minimize number of product terms)



Examples to Illustrate Terms

		C		
	0	X	1	0
	1	1	1	0
A	1	0	1	1
	0	0	1	1
		D		

6 prime implicants:

ABD' , $A'D$, AC , $A'BC'$, CD , $BC'D'$

essential

minimum cover: $AC + A'D + BC'D'$

5 prime implicants:

BD , ABC , $AC'D$, $A'BC'$, $A'CD$

essential

minimum cover: 4 essential implicants

		C		
	0	0	1	0
	1	1	1	0
A	0	1	1	1
	0	1	0	0
		D		




Prime Implicants

Any single 1 or group of 1s in the Karnaugh map of a function F is an implicant of F .

A product term is called a prime implicant of F if it cannot be combined with another term to eliminate a variable.

Example:

 

If a function F is represented by this Karnaugh Map. Which of the following terms are implicants of F , and which ones are prime implicants of F ?

- (a) $A'B'C$
- (b) BD
- (c) $A'B'C'D'$
- (d) $A'C$
- (e) $A'B'D'$

Implicants:
(a),(c),(d),(e)


Prime Implicants:
(d),(e)




Essential Prime Implicants

A product term is an essential prime implicant if there is a minterm that is only covered by that prime implicant

 The minimal sum-of-products form of F must include all the essential prime implicants of F



 (a) Essential prime implicants BD and $B'D'$



(b) Prime implicants $CD, B'C, AD,$ and AB'

Fig. 3-11 Simplification Using Prime Implicants



Summary

- Karnaugh map allows us to represent functions with new notation
- Representation allows for logic reduction
 - Implement same function with less logic
- Each square represents one minterm
- Each circle leads to one product term
- Not all functions can be reduced
- K-maps of four literals were considered (Larger examples exist)
- Don't care conditions help minimize functions
- Result of minimization is a minimal sum-of-products
- Result contains prime implicants
- Essential prime implicants are required in the implementation



COE211: Digital Logic Design

Combinational Circuits



Outlines

- Introduction
- Combinational Circuit Analysis
- Combinational Circuit Design
- Binary Adders and Subtractors
- Binary Decoders and Encoders
- Magnitude Comparator
- Binary Multiplexers
- Three-state Gates




Introduction

Digital Circuits have two types of circuits:

 
1. Combinational Circuits

- Outputs depend on the inputs only
- Memoryless circuits



 2. Sequential Circuits

- Current outputs depend on the inputs and the previous state (outputs).
- Use memory to store the previous state.





Introduction (Cont.)

Combinational Circuits:

- **Combinational Circuit analysis:**
 - In the analysis we are interested in determining the function of a given combination circuit.

- **Combinational Circuit design:**
 - In the design we are interested in developing a combinational circuit based on a given function.



Combinational Circuit Analysis

3/9/2020

COE211: Digital Logic Design

5



Combinational Circuit Analysis

Circuit analysis can be achieved by either one of the following two methods:


- Determining the output functions as algebraic expressions.
- Determining the truth table of the output functions.



Circuit Analysis steps

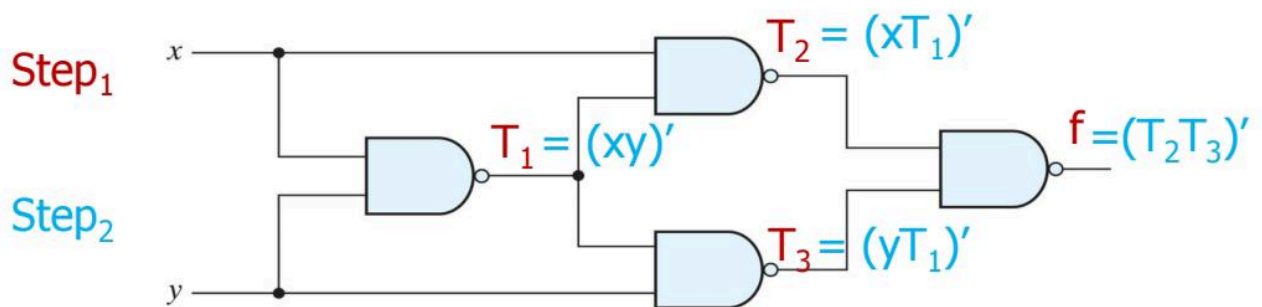1. Label all gate outputs with symbols.
2. Determine Boolean function at the output of each gate.
3. Express functions in terms of input variables
4. Simplify

■ **Example:** Find the output function of the following circuit.




Step₃

$$f = (T_2T_3)' = ((xT_1)'(yT_1)')' = (xT_1) + (yT_1) = x(xy)' + y(xy)'$$
$$= x(x' + y') + y(x' + y') = xy' + x'y = x \oplus y$$




Solution using Truth Table

 

x	y	$T_1=(xy)'$	$T_2=(xT_1)'$	$T_3=(yT_1)'$	$f=(T_2T_3)'$
0	0	1	1	1	0
0	1	1	1	0	1
1	0	1	0	1	1
1	1	0	1	1	0



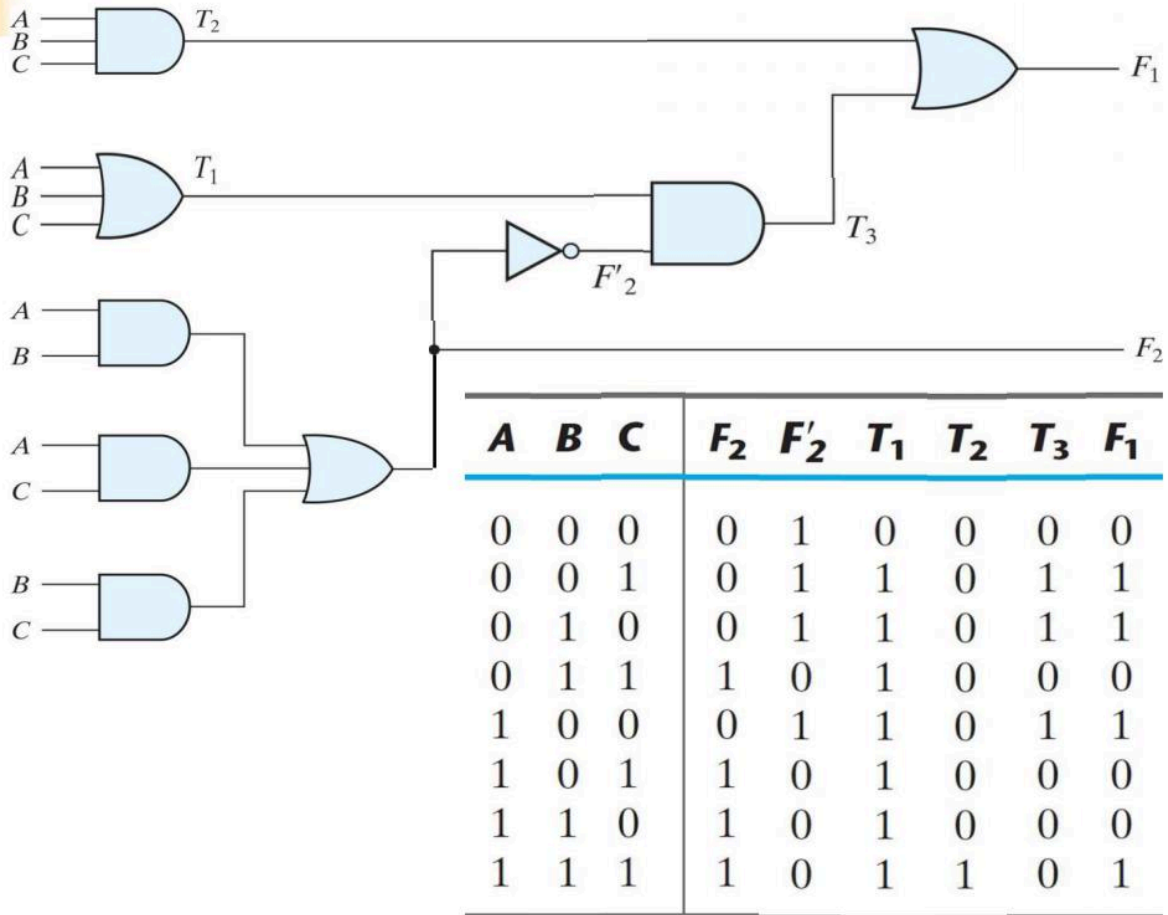
Example 2: Find the functions of the following Circuit using Truth Table





 Exercise

What are the output functions F_1 and F_2 of the following logic circuit?



Copyright ©2013 Pearson Education, publishing as Prentice Hall



Combinational Circuit Design

3/9/2020

COE211: Digital Logic Design

11



Design of Combinational Circuits

Four main steps in designing a combinational circuit:

1. Determine the number of inputs and outputs and give them symbols.
2. Derive the related Truth Table.
3. Simplify each output.
4. Draw logic diagram and verify correctness.



Design of Combinational Circuits (Cont.)

Example 1: Design a combinational logic circuit that detects odd inputs which are in the rang from 0 to 7.

Solution:

Step 1: 3 inputs (A, B, and C) and one output (F).

Step 2: Truth table

Step 3: Simplify

A\BC	00	01	11	10
0	0	1	1	0
1	0	1	1	0

$$F = C$$

A	B	C	F
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1



Design of Combinational Circuits (Cont.)

Example 2: Develop a combinational circuit that converts a BCD digit into a Excess-3 code.

Solution:

Step 1:

- Inputs: BCD digit
(4 inputs: A, B, C, D)
- Outputs: Excess-3 code
(4 outputs: w, x, y, z).

Step 2: Truth table

A	B	C	D	w	x	y	z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0



Example 2 (Cont.)

Step 3: Outputs' Simplification

AB\CD	00	01	11	10
00	0	0	0	0
01	0	1	1	1
11	x	x	x	x
10	1	1	x	x

$$w = A + BC + BD$$

AB\CD	00	01	11	10
00	0	1	1	1
01	1	0	0	0
11	x	x	x	x
10	0	1	x	x

$$x = B'C + B'D + BC'D'$$

AB\CD	00	01	11	10
00	1	0	1	0
01	1	0	1	0
11	x	x	x	x
10	1	0	x	x

$$y = C'D' + CD$$


AB\CD	00	01	11	10
00	1	0	0	1
01	1	0	0	1
11	x	x	x	x
10	1	0	x	x

$$z = D'$$



Example 2 (Cont.)

Step 4: Circuit Drawing

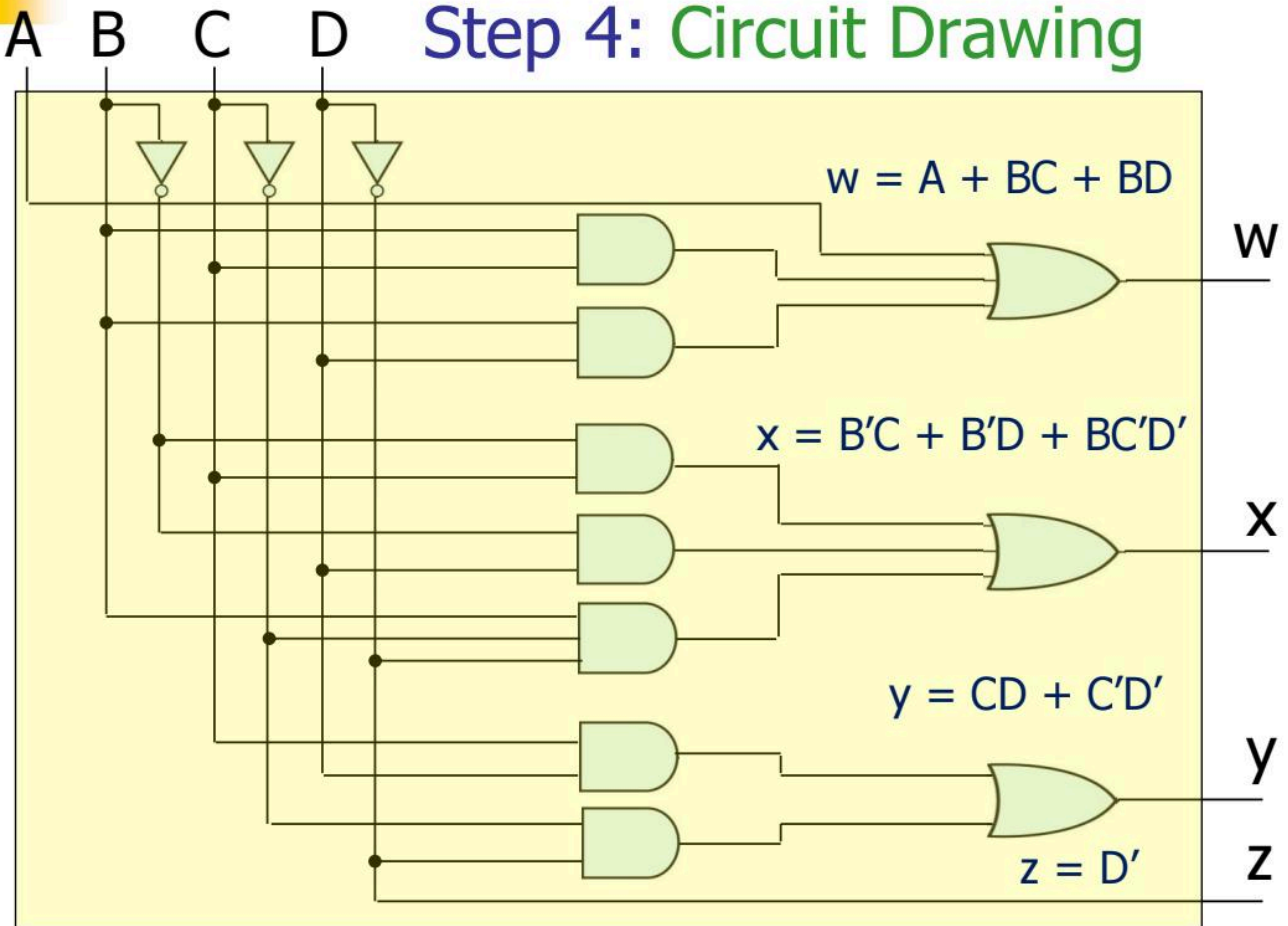



Binary Adders and Subtractors

3/9/2020

COE211: Digital Logic Design

17



Half Adder

Add two binary numbers


- **x, y** → single bit inputs
- **S** → single bit sum
- **C** → carry out

Half Adder

x	y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0


Dec Binary

1	1
+1	+1
<hr/>	
2	10

 

$$(a) S = xy' + x'y$$

$$C = xy$$

 

$$(b) S = x \oplus y$$

$$C = xy$$



Multiple-bit Addition

Consider adding a 4-bit number to a 4-bit number:
(single-bit adder are used for each bit position)

	A_3	A_2	A_1	A_0		B_3	B_2	B_1	B_0	
A	0	1	0	1		B	0	1	1	1
	1	1	1							
A	0	1	0	1		C_{i+1}		C_i		
B	0	1	1	1				A_i		
	<hr/>							$+B_i$		
	1	1	0	0				S_i		

Each bit position creates a sum and carry




Full Adder


Full adder includes a carry-in **z**

Full Adder

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

 


$$S = x'y'z + x'yz' + xy'z' + xyz$$

 

$$C = xy + xz + yz$$



Full Adder (cont.)

 



Full Adder (cont.)

The AND/OR representations of **S** and **C** can be reduced into XORs as follows:

$$\begin{aligned} S &= x'y'z + x'yz' + xy'z' + xyz \\ &= z(x'y' + xy) + z'(x'y + xy') = z(x \odot y) + z'(x \oplus y) \\ &= z(x \oplus y)' + z'(x \oplus y) = z \oplus x \oplus y \end{aligned}$$

$$\begin{aligned} C &= xy + x'yz + xy'z \\ &= xy + z(x'y + xy') \\ &= xy + z(x \oplus y) \end{aligned}$$

Therefore, the final equations are:


$$S = z \oplus x \oplus y$$

$$C = xy + z(x \oplus y)$$




Full Adder (cont.)
 
$$S = z \oplus x \oplus y \quad \text{and} \quad C = xy + z(x \oplus y)$$



 Therefore, the full adder can be constructed from two half adders and an OR gate.






Full Adder (cont.)


Putting it all together

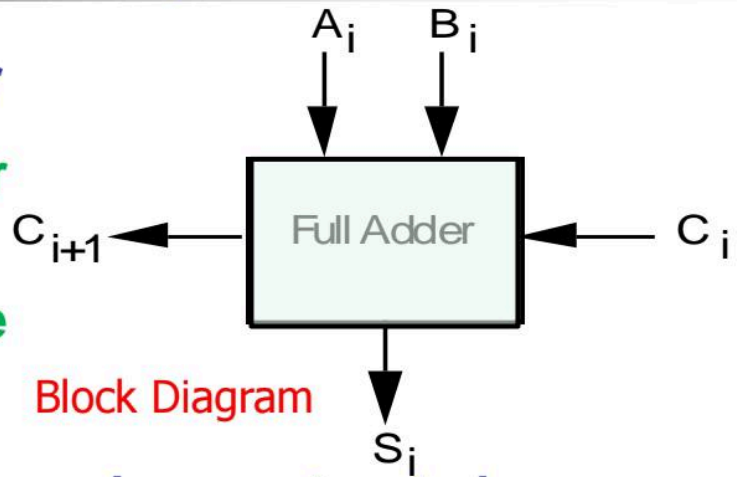- Single-bit full adder
- Common piece of computer hardware



Block Diagram

 Accordingly, 4-bit Adder can be constructed as:





Subtractor


- Subtracting a number is similar

- Perform 2's complement
- Perform addition

- Can we augment the adder with 2's complement hardware?

$$\begin{array}{r} A_3 \ A_2 \ A_1 \ A_0 \\ - \ B_3 \ B_2 \ B_1 \ B_0 \\ \hline A_3 \ A_2 \ A_1 \ A_0 \\ + \ B'_3 \ B'_2 \ B'_1 \ B'_0 \\ + \qquad \qquad \qquad 1 \\ \hline \end{array}$$


2's complement

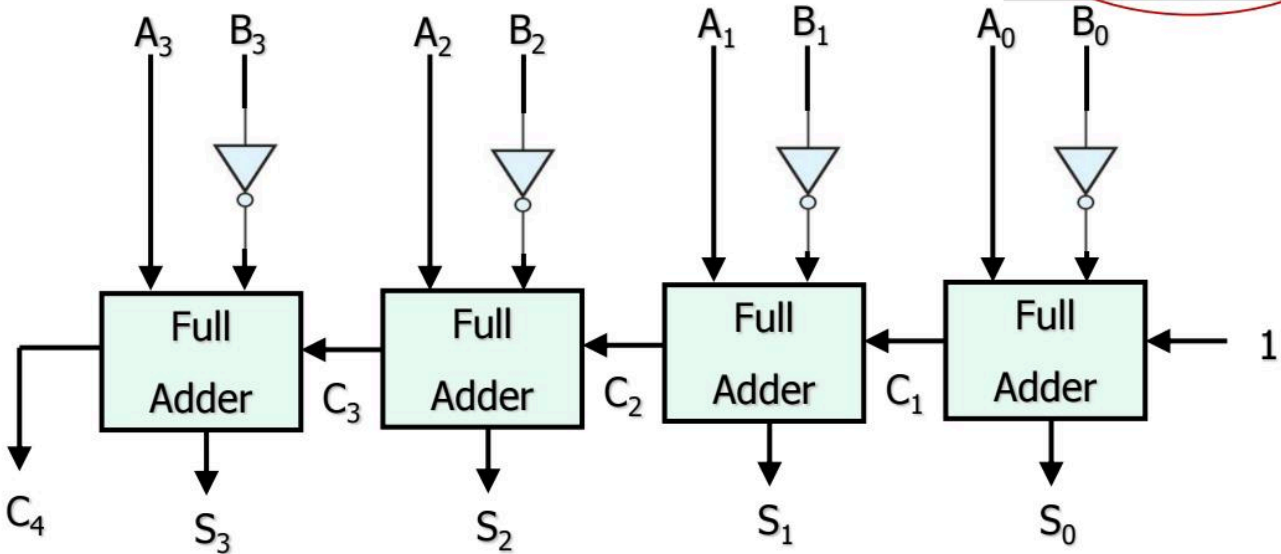



Adder-Subtractor

 - 4-bit Adder-subtractor (with overflow detection).
 - When $C_0 = 0$, the circuit is used as an Adder.
 - When $C_0 = 1$, the circuit is used as a Subtractor.





Overflow in 2's Complement Addition

When two values of the same sign are added:

- Result won't fit in the number of bits provided
- Result has the opposite sign

00	01	11	10	00	11
0010	0011	1110	1101	0010	1110
0011	0110	1101	1010	1100	0100
-----	-----	-----	-----	-----	-----
0101	1001	1011	0111	1110	0010
+2	+3	-2	-3	2	-2
<u>+3</u>	<u>+6</u>	<u>-3</u>	<u>-6</u>	<u>-4</u>	<u>+4</u>
5	-7	-5	7	-2	2
	OFL		OFL		



Summary

- Addition and subtraction are fundamental to computer systems
- Create a single bit adder/subtractor
 - Chain the single-bit hardware together to create bigger designs
- The approach is called ripple-carry addition
 - Can be slow for large designs
- Overflow is an important issue for computers
 - Processors often have hardware to detect overflow




Binary Decoder and Encoder




Binary Decoder

 - Black box with n input lines and 2^n output lines.
- Only one output is a 1 for any given input.






2-to-4 Binary Decoder

 



A	B	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

 

Note: Each output is a 2-variable minterm ($A'B'$, $A'B$, AB' or AB)



3-to-8 Binary Decoder

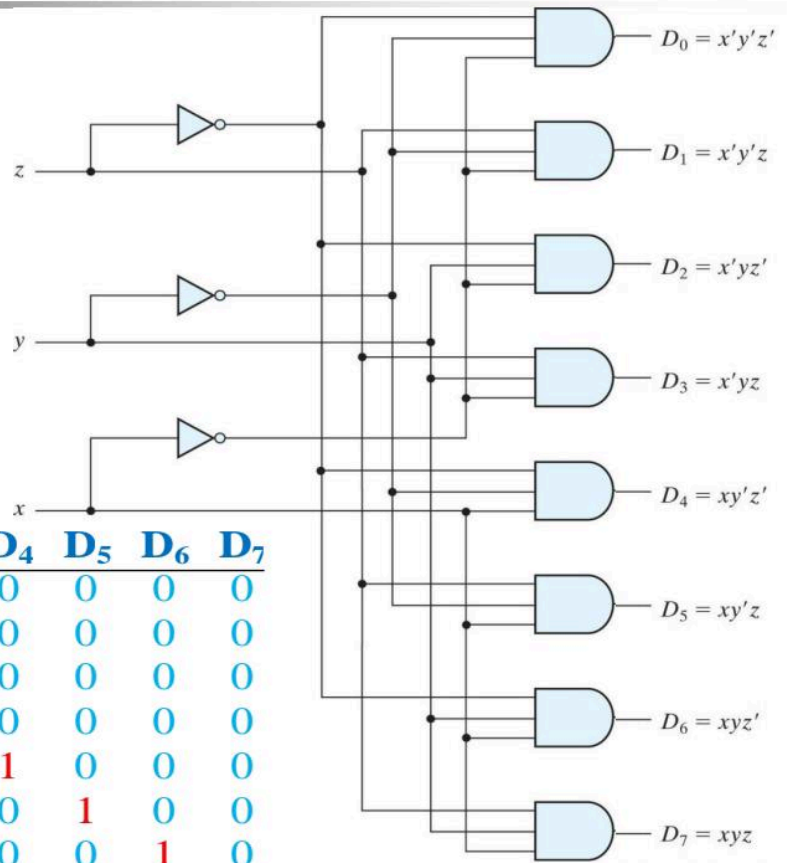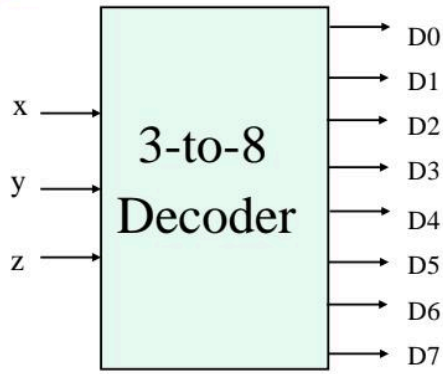


x	y	z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1



Building a binary decoder with NAND gates

- 2-to-4 decoder with enable
- Add enable signal (E)
- Note:** using NAND Gates makes only one 0 be active if the enable $E = 0$.


E	A	B	D_0	D_1	D_2	D_3
1	X	X	1	1	1	1
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	1

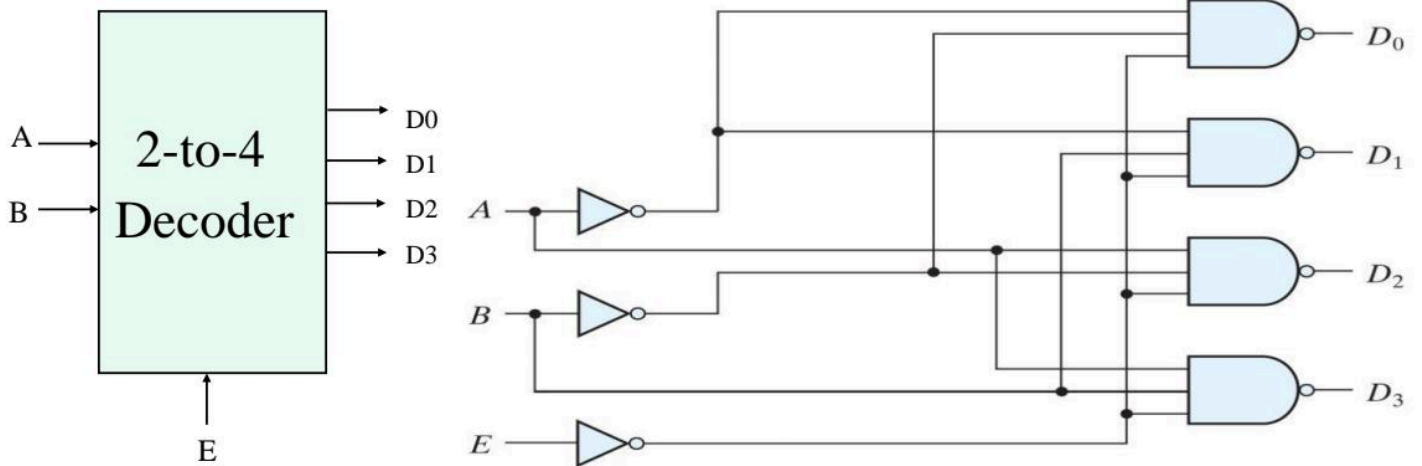



Use two 3-to-8 decoders to make 4-to-16 decoder

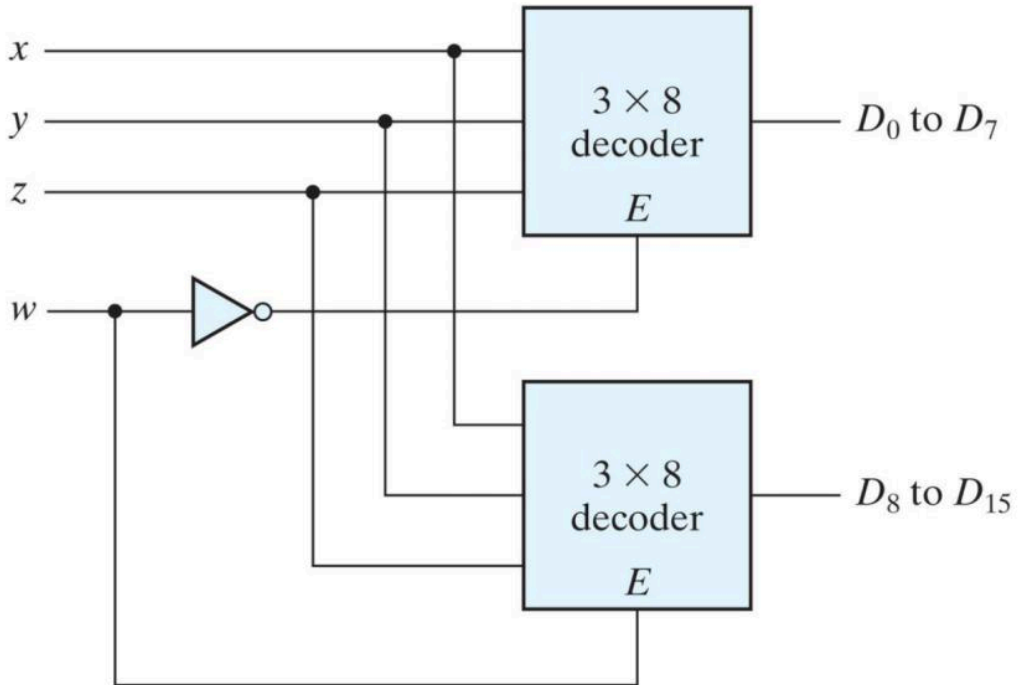- The enable is used as the 4th line.
- In this case, only one decoder can be active at a time.





Implementing Functions Using Decoders

- Any n -variable logic function can be implemented using a single n -to- 2^n decoder to generate the minterms.
 - OR gate forms the sum
 - The output lines of the decoder corresponding to the minterms of the function are used as inputs to the OR gate
- Any combinational circuit with n inputs and m outputs can be implemented with an n -to- 2^n decoder with m OR gates.
- Suitable when a circuit has many outputs, and each output function is expressed with few minterms.




Example

Implement the function of the Full adder using a decoder.

Sum: $S(x, y, z) = \Sigma (1,2,4,7)$

Carry: $C(x, y, z) = \Sigma (3,5,6,7)$

x	y	z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

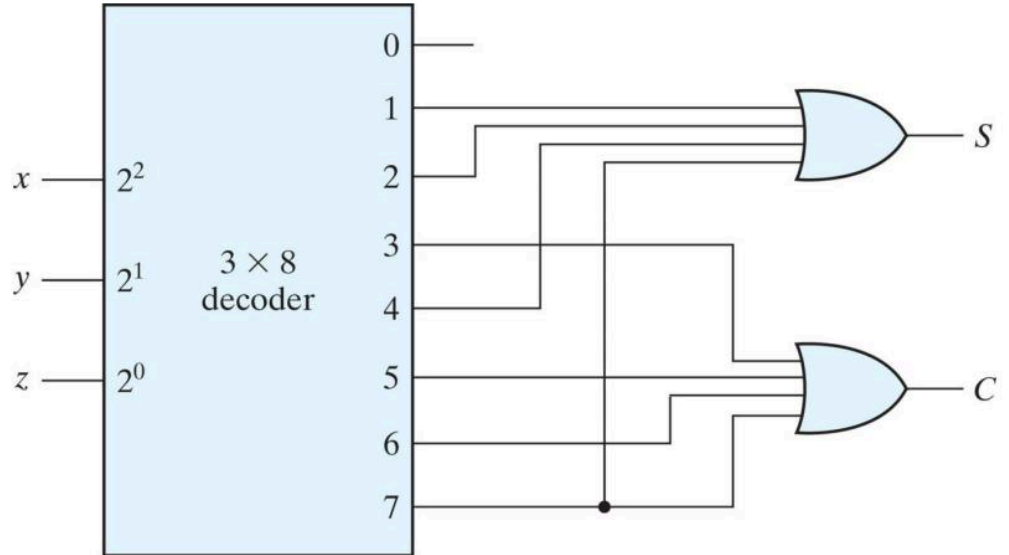


Note: if you have the function, you do not need to construct the truth table.



Binary Encoder

 - If the a decoder's output code has fewer bits than the input code, the device is usually called an encoder.
 - e.g. 2^n -to- n
- The simplest encoder is a 2^n -to- n binary encoder
 - One of 2^n inputs = 1
 - Output is an n -bit binary number






8-to-3 Encoder

Truth Table of an Octal-to-Binary Encoder

Inputs								Outputs		
D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7	x	y	z
1	0	0	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	1	0	0	0	1	0	0
0	0	0	0	0	1	0	0	1	0	1
0	0	0	0	0	0	1	0	1	1	0
0	0	0	0	0	0	0	1	1	1	1

 


Note: At any one time, only one input line has a value of 1.



Encoder Application (Monitoring Unit)

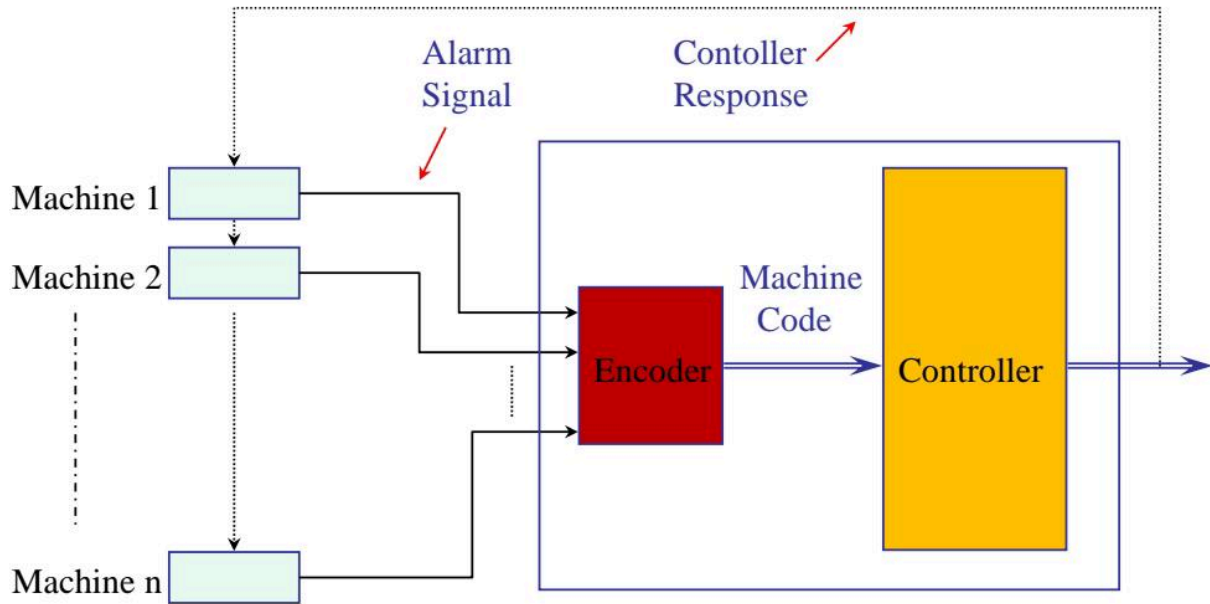- Encoder identifies the requester and encodes the value.
- Controller accepts digital inputs.





Summary

- Decoders allow for generation of a single binary output from an input binary code.
- For an n -input binary decoder there are 2^n outputs.
- Decoders are widely used with memory.
- Encoders can be used for data compression.



Binary Magnitude Comparators

3/9/2020

COE211: Digital Logic Design

41



Magnitude Comparator

- Compares two numbers: A and B
 - Result: $A > B$, $A = B$, or $A < B$
- Truth table entries for n -bit numbers = 2^{2n} entries
 - Impractical for design
- How can we determine that two numbers are equal?
 - $A_3 A_2 A_1 A_0$ and $B_3 B_2 B_1 B_0$ are equal **iff**
 - $A_3 = B_3$ and $A_2 = B_2$ and $A_1 = B_1$ and $A_0 = B_0$
- New function: x_i indicates if $A_i = B_i$
 - $x_i = A_i B_i + A'_i B'_i$ (X-NOR)
 - Thus, $(A = B) = x_3 x_2 x_1 x_0$
 - What about $A < B$ and $A > B$?



Magnitude Comparator (cont.)

- $A > B$
 - How can we tell that $A > B$?
 - Look at MSB where A and B differ
 - ✓ If $A = 1$ and $B = 0$, then $A > B$
 - ✓ If not, then $A \leq B$
 - Assume $n = 4$
 - $(A > B) = A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$
- $A < B$
 - The same as $A > B$ but A and B are exchanged.
 - $(A < B) = A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$


Note: The comparison must be started from MSB.



Magnitude Comparator (cont.)

- $(A > B) = A_3 B'_3 + x_3 A_2 B'_2 + x_3 x_2 A_1 B'_1 + x_3 x_2 x_1 A_0 B'_0$
- $(A < B) = A'_3 B_3 + x_3 A'_2 B_2 + x_3 x_2 A'_1 B_1 + x_3 x_2 x_1 A'_0 B_0$

- $(A = B) = x_3 x_2 x_1 x_0$

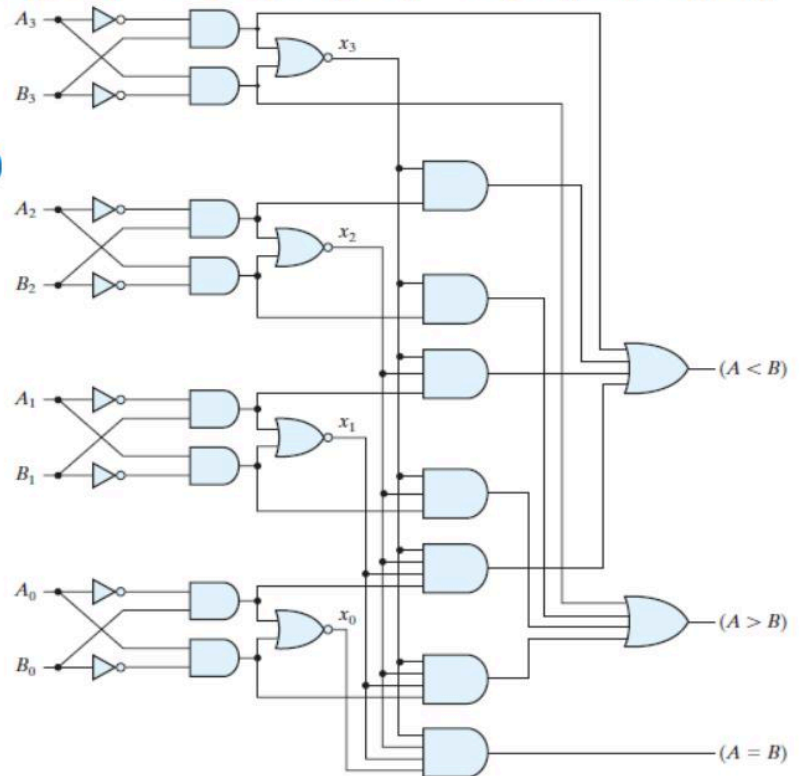





Binary Multiplexers



Binary Multiplexers

  - Select an input value with one or more select bits
- Use for transmitting data
- Allow for conditional transfer of data
- Sometimes called a **MUX**
- **Example: 2-to-1 MUX**






Multiplexers (cont.)

4-to-1 Multiplexer

- 4 input lines (I_0, I_1, I_2, I_3)
- 2 selection lines (S_0, S_1)
- One output line (Y)
- Function table

S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

 




Multiplexers (cont.)

■ Quadruple 2-to-1 MUX

- 4-bit inputs
- 4-bit outputs
- one selection bit (S)
- Enable bit (E)

E	S	Output Y
1	X	all 0's
0	0	select A
0	1	select B


Function table

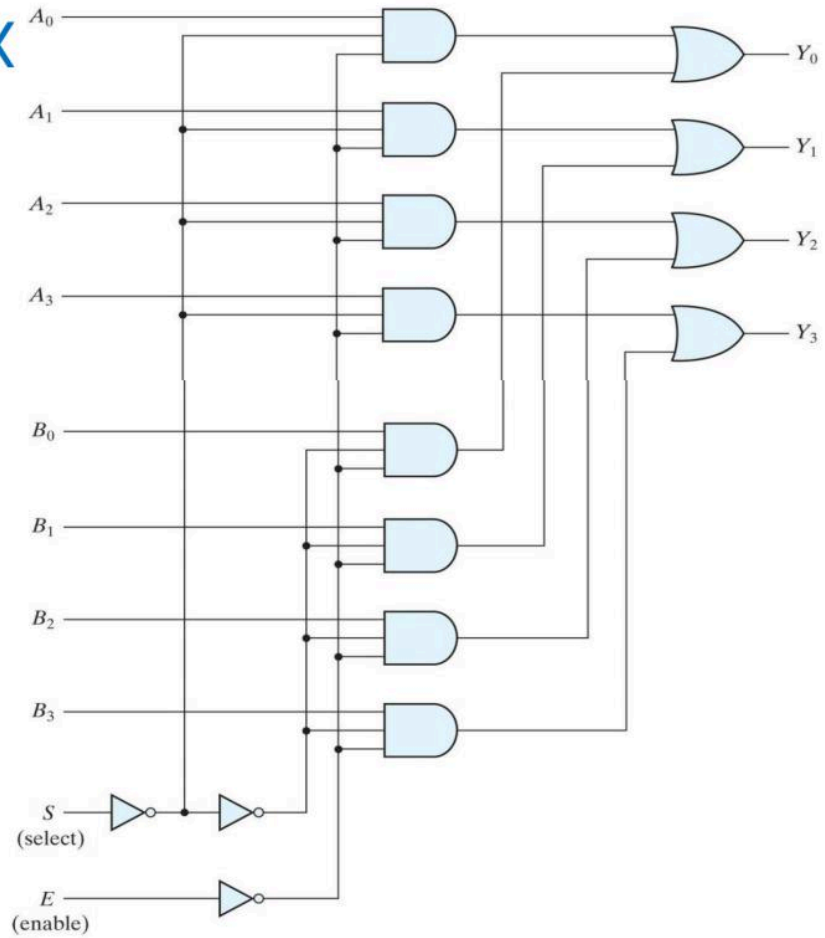



Implementing Boolean Functions with MUXs

 - Example: Implement the Boolean function $F(x, y, z) = \Sigma(1, 2, 6, 7)$ using 4 x 1 MUX.



S_1	S_0	x	y	z	F	
0	0	0	0	0	0	
0	0	0	1	1	1	$I_0 = Z$
0	1	0	0	1	1	$I_1 = z'$
0	1	1	1	0	0	
1	0	0	0	0	0	$I_2 = 0$
1	0	1	0	1	0	
1	1	0	0	1	1	$I_3 = 1$
1	1	1	1	1	1	


- Set "data" input lines of multiplexer to function values
- Connect input variable to "select" inputs
- Set the inputs of multiplexer.



Implementing a 4-Input Function with a MUX

- Example: Implement the Boolean function $F(A, B, C, D) = \Sigma(1, 3, 4, 11, 12, 13, 14, 15)$ using 8×1 MUX.

S_2 ↓ A	S_1 ↓ B	S_0 ↓ C	D	F	
0	0	0	0	0	$I_0 = D$
0	0	0	1	1	$I_1 = D$
0	0	1	0	0	$I_2 = D'$
0	0	1	1	1	
0	1	0	0	1	
0	1	0	1	0	$I_3 = 0$
0	1	1	0	0	$I_4 = 0$
0	1	1	1	0	
1	0	0	0	0	$I_5 = D$
1	0	0	1	0	
1	0	1	0	0	
1	0	1	1	1	
1	1	0	0	1	$I_6 = 1$
1	1	0	1	1	
1	1	1	0	1	$I_7 = 1$
1	1	1	1	1	

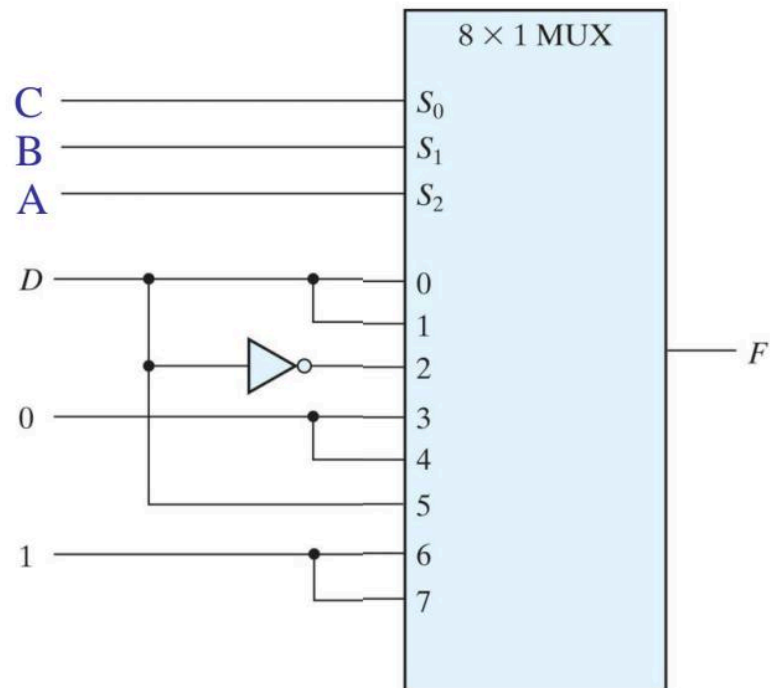




Three-state Gate




Three-state Gate

 - Output: 0, 1, and high-impedance (open circuit)
- If the select input (E) is 0, the three-state gate has **no output**



E	x
0	Hi-Z
1	A

Opposite true here,
No output if E is 1

 


\bar{E}	x
0	A
1	Hi-Z




Three-state Gate (cont.)

 - Multiplexers can be constructed with three-state gates.
- Two examples



(a) 2-to-1-line mux

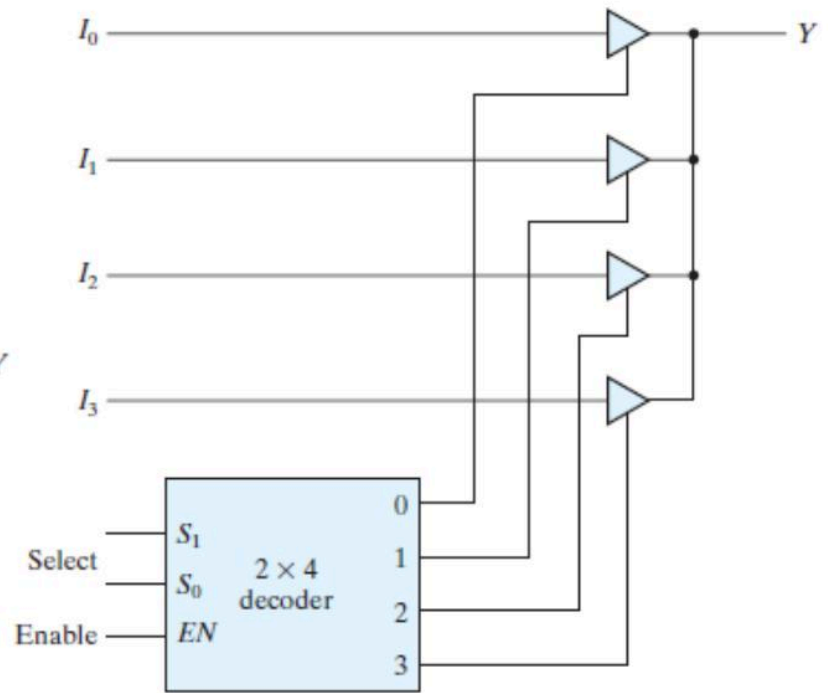

(b) 4-to-1-line mux



Summary

- Magnitude comparators allow for data comparison
 - Can be built using AND-OR gates
 - Greater / Less than requires more hardware than equality
- Multiplexers are fundamental digital components
 - Can be used for implementing logic functions
 - Useful for datapaths
 - Scalable
- Tristate buffers have three types of outputs
 - 0, 1, high-impedence (Z)
 - Useful for datapaths



COE211: Digital Logic Design

CH5: Synchronous Sequential Logic

Part 1: Latches and Flip-Flops





So Far ...

- Logical operations which respond to *combinations* of inputs to produce an output
 - Call these *combinational logic* circuits
- For example, we can add two numbers but:
 - No way to add two numbers, *then* add a third (a *sequential* operation)
 - No way to remember or *store* information after inputs have been removed
- To do this, we need *sequential logic* capable of storing intermediate (and final) results



Sequential Circuits

 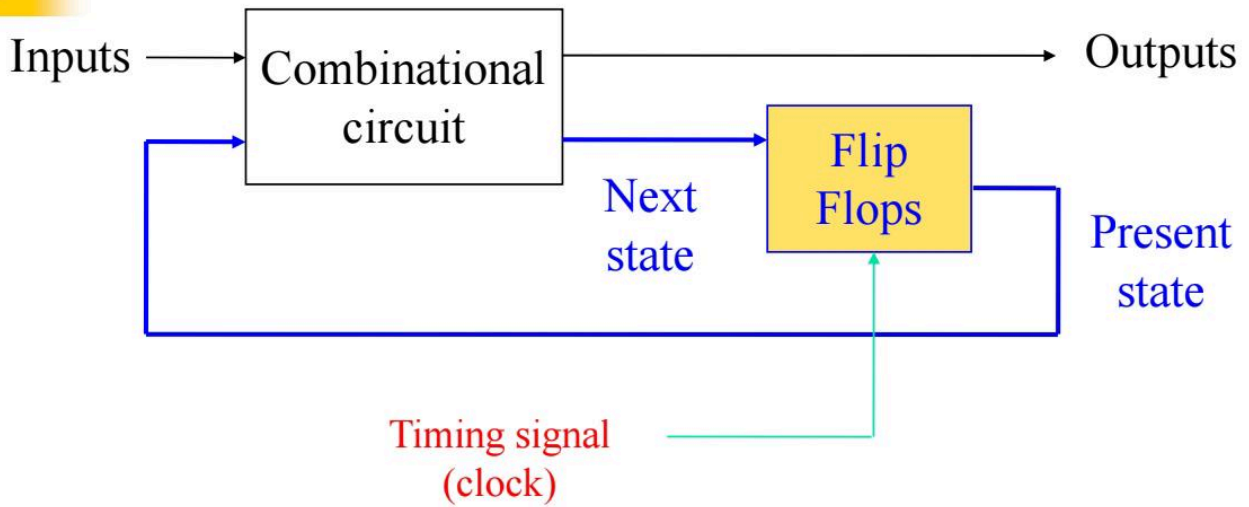

- synchronizes when current state changes should happen
- keeps system well-behaved
- makes it easier to design and build large systems



Storage Elements

- Binary storage device capable of storing one bit
- Latch = level-sensitive device
 - Control signal: Enable
 - State changes with input when enabled (e.g., when Enable = 1)
 - Holds last input value when disabled (when Enable = 0)
- Flip-flop = edge-triggered device
 - Control signal: periodic Clock
 - State of flip-flop can only change during clock transition
 - Example: Flip-flops change on rising/falling edge of clock
- Why change on an edge?
 - Couldn't we change state while clock is 1?
 - That would be a latch!
- Edge is moment in time, state is duration conditions



Level-sensitive vs Edge-triggered

- Latches are level-sensitive



(a) Response to positive level

- Flip-flops are edge-sensitive



(b) Positive-edge response



(c) Negative-edge response




Latches

- Characteristics
 - Can store one bit of binary information
 - Level-sensitive devices, asynchronous
- SR Latch
 - Named after functionality: S = set, R = reset
 - Specification:
 - Inputs: S and R
 - Outputs: Q and Q'
- SR Latch Operation:
 - Q=1 and Q'=0 when in set state
 - Q=0 and Q'=1 when in reset state
 - Inputs should be 0 unless pulse on S or R sets or resets latch




Cross-coupled Inverters

A stable value can be stored at inverter outputs

 


State 1

 



State 2



SR Latch with NORs

 

  
- *Set* and *Reset* are stable states
 - If $S=0$ and $R=0$, then state will not change by itself






RS Latch with NANDs

 - RS latch is made from two **cross-coupled NANDs**
- Sometimes called $\bar{R}\bar{S}$ latch
- Usually $\bar{S}=1$ and $\bar{R}=1$






RS Latches

 

(a) Logic diagram

S	R	Q	\bar{Q}
1	0	1	0
0	0	1	0
Set state			
0	1	0	1
0	0	0	1
Reset state			
1	1	0	0
Undefined			

(b) Function table

 

(a) Logic diagram


S	R	Q	\bar{Q}
0	1	1	0
1	1	1	0
Set state			
1	0	0	1
1	1	0	1
Reset state			
0	0	1	1
Undefined			

 (b) Function table



RS Latch with control input

- Avoid uncontrolled latch changes
- **C = 0** disables all latch state changes
- Control signal enables data change when **C = 1**



(a) Logic diagram

C	S	R	Next state of Q
0	X	X	No change
1	0	0	No change
1	0	1	$Q = 0$; Reset state
1	1	0	$Q = 1$; set state
1	1	1	Indeterminate

(b) Function table

Fig. 5-5 SR Latch with Control Input



D Latch


- How to remove state for $S=1, R=1$?
- Solution
 - Just use one input pin D to indicate set or reset
 - Enable bit (En) ensures that latch is only set when intended

- D latch

- Inputs:
 - D (data)
 - En (enable)

En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

- Circuit:

 




D Latch in Operation

- Removes disallowed R,S combination
 - D latch forwards data while $En=1$
 - D latch holds data when $En=0$



En	D	Next state of Q
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

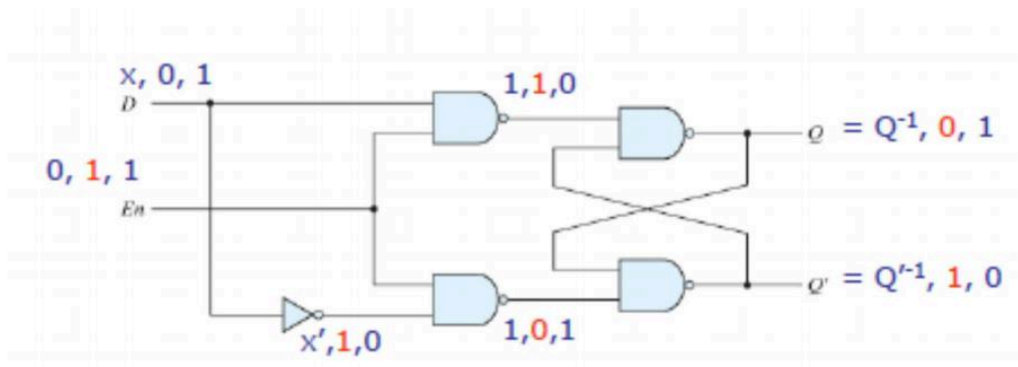



D Latch

  - **Z** only changes when **E** is high
- If **E** is high, **Z** follows **X**






- If **E = 0**, the D latch stores data indefinitely regardless of input D values
- Forms basic storage element in computers



Symbols for Latches

   - RS latch, based on NOR gates
- R'S' latch, based on NAND gates
- D latch can be based on either NOR or NAND
- D latch, sometimes called transparent latch





Summary

- Latches are based on combinational gates (e.g. NAND, NOR)
- Latches store data even after data input has been removed
- RS latches operate like cross-coupled inverters with control inputs (S = Set, R = Reset)
- With additional gates, a RS latch can be converted to a D latch (D stands for Data)
- D latch operation is simple
 - When $C = 1$, data input D stored in latch and $Q = D$
 - When $C = 0$, data input D is ignored and $Q =$ previous latch value

Sec: 5.3


Sequential Circuits: Flip Flops





D Latch - Summary

- D latch circuit

 


<i>Ea</i>	<i>D</i>	Next state of <i>Q</i>
0	X	No change
1	0	$Q = 0$; reset state
1	1	$Q = 1$; set state

- Data is stored while clock is high



 
- How can we build a flip-flop that stores on edge transition?





Edge-triggered D Flip-Flop

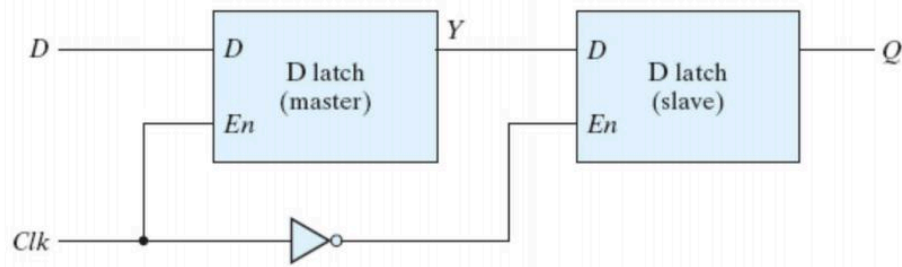
- Construct D flip-flop from two latches:




- Primary latch:
 - Reads value of D while CLK is high
 - Is disabled when clock is low
- Secondary latch:
 - Is disabled when CLK is high (i.e., holds previous value)
 - Takes value from master on negative edge of clock



Clocked D Flip-Flop

 


D	CLK	Q
0	↑	0
1	↑	1

 



Positive and Negative Edge D Flip-Flops

 - There exist positive and negative edge trigger D FF
- **Bubbled *Clock (C)* means negative edge trigger**



(a) Positive-edge

(a) Negative-edge

Fig. 5-11 Graphic Symbol for Edge-Triggered *D* Flip-Flop

We may need other FFs to *synchronously* set or reset the FF state and/or complement the previous state







Positive Edge-Triggered J-K Flip-Flop

- Created from D FF
- K resets
- J sets
- J=K=1 inverts Q

J	K	CLK	Q	Q'
0	0		Q_0	Q_0'
0	1		0	1
1	0		1	0
1	1		Q_0'	Q_0

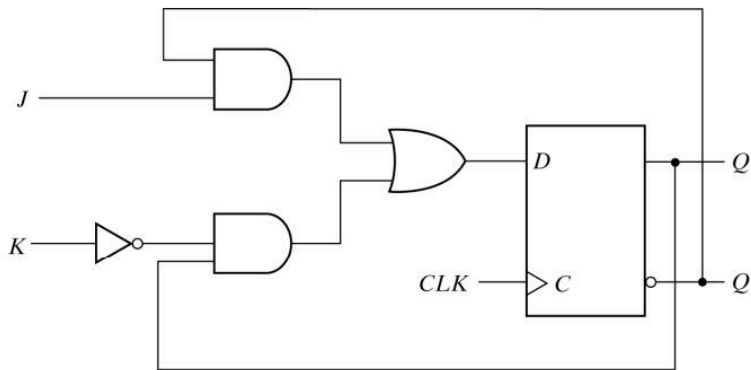

(a) Circuit diagram

 


(b) Graphic symbol

Fig. 5-12 JK Flip-Flop




Clocked J-K Flip Flop

 J: set, K: reset, if $J=K=1$ then toggle output



J	K	CLK	Q
0	0	↑	Q_0 (no change)
1	0	↑	1
0	1	↑	0
1	1	↑	Q_0 (toggles)

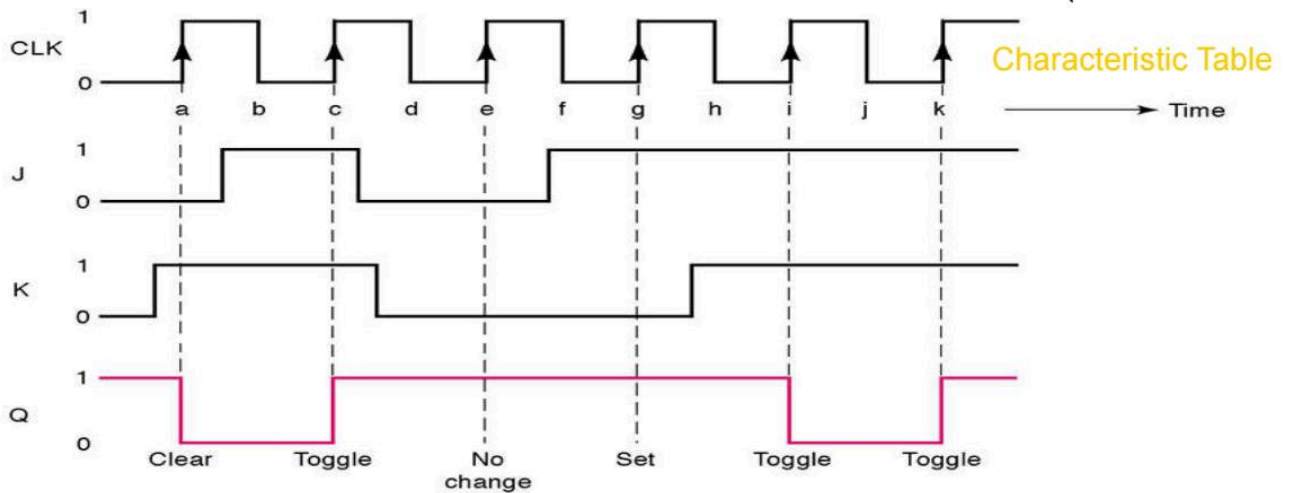



Positive Edge-Triggered T Flip-Flop

- Created from JK or D F.F.
- $T=0 \rightarrow$ No change
- $T=1 \rightarrow$ invert Q

T	CLK	Q	Q'
0		Q_0	Q_0'
1		Q_0'	Q_0


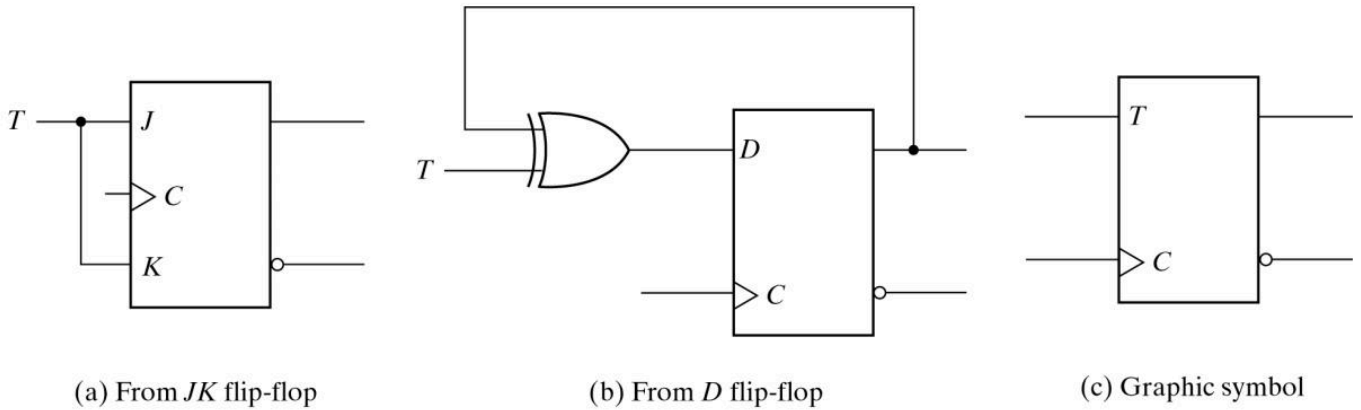


Fig. 5-13 T Flip-Flop

 


Characteristic Table and Equation




D	Q(t+1)
0	0
1	1

$$Q(t+1) = D$$

 

J	K	Q(t+1)
0	0	Q(t)
0	1	0
1	0	1
1	1	Q'(t)

$$Q(t+1) = JQ'(t) + K'Q(t)$$

 


T	Q(t+1)
0	Q(t)
1	Q'(t)

$$Q(t+1) = TQ' + T'Q$$



Asynchronous Inputs

 - J, K are *synchronous* inputs
 - Effects on the output are synchronized with the *CLK* input
- *Asynchronous* inputs operate independently of the clock and synchronous inputs
 - Set/reset the FF to 1/0 states *at any time*





PRESET	CLEAR	FF response
1	1	Clocked operation*
0	1	Q = 1 (regardless of CLK)
1	0	Q = 0 (regardless of CLK)
0	0	Not used

*Q will respond to J, K, and CLK



Asynchronous Inputs

 
 


Point	Operation
a	Synchronous toggle on NGT of CLK
b	Asynchronous set on $\overline{PRE} = 0$
c	Synchronous toggle
d	Synchronous toggle
e	Asynchronous clear on $\overline{CLR} = 0$
f	\overline{CLR} over-rides the NGT of CLK
g	Synchronous toggle



Asynchronous Inputs

  - Reset signal (R) is active low
 - R = 0 clears the output Q
- This event can occur at any time, regardless of the value of the CLK




R	C	D	Q	Q'
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0



Parallel Data Transfer

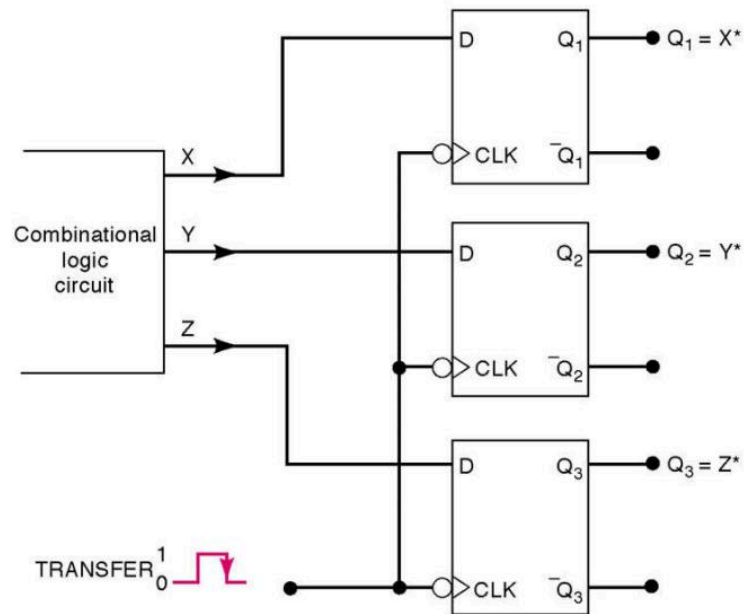- Flip flops store outputs from combinational logic
- Multiple flops can store a collection of data



*After occurrence of NGT



Summary

- Flip flops are powerful storage elements
 - They can be constructed from gates and latches!
- D flip flop is simplest and most widely used
- Asynchronous inputs allow for *clearing* and *presetting* the flip flop output
- Multiple flip flops allow for data storage
 - The basis of computer memory!
- Combine storage and logic to make a computation circuit